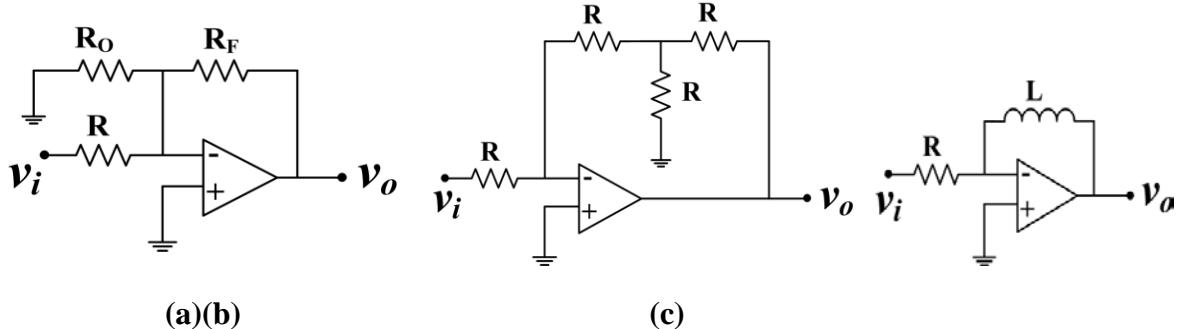
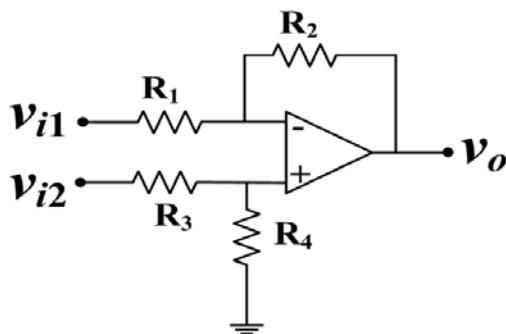


3rd October, 2016**Home Assignment -9**

1. For the circuits shown in **Fig. 1**, determine ' v_o ' in terms of ' v_i '. Assume that the op-amps are ideal.

**Fig. 1**

2. Determine ' v_o ' in terms of ' v_i ' for the difference amplifier, using an ideal op-amp, as shown in **Fig. 2**, assuming that both the inputs v_{i1} and v_{i2} are connected to a common input v_i ($v_i = v_{i1} = v_{i2}$). This is known as **common mode gain** ($A_{cm} = \frac{v_o}{v_i}$) of this difference amplifier. Also, calculate generalized expression for ' v_o ' in terms of ' v_{i1} ' and ' v_{i2} '. Show that if $\frac{R_2}{R_1}$ is chosen to be equal to $\frac{R_4}{R_3}$, then A_{cm} becomes zero and differential mode gain ($A_{dm} = \frac{v_o}{v_{i2} - v_{i1}}$) becomes $\frac{R_2}{R_1}$. Now assuming that the resistor ratio $\frac{R_2}{R_1}$ is 1% less than $\frac{R_4}{R_3}$, determine the **common mode rejection ratio(CMRR)** of the circuit in dB. The values of R_3 and R_4 are $10\text{ k}\Omega$ and $100\text{ k}\Omega$ respectively.

**Fig. 2**

3. Design an ideal op-amp to produce the output $v_o = 2v_{i1} + 3v_{i2} - 4(v_{i3} + 5v_{i4})$. All the input signals are in phase. Resistor values must be in between $1\text{ k}\Omega$ and $100\text{ k}\Omega$.

4. For the circuit shown in **Fig.3**, if $v_i = 1\text{V}$, determine v_o and all the branch currents i_1 , i_2 , i_o and i_L , assuming the op-amp to be ideal. Repeat the same for $v_i = -1\text{ V}$. Also, determine the amount of current supplied (or sunk) by the op-amp output in each case.

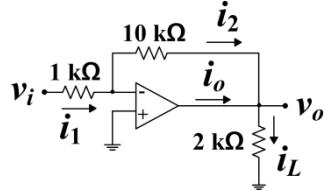


Fig. 3

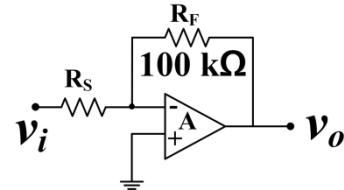


Fig. 4

5. An inverting op-amp shown in **Fig.4** has to be designed to have a gain of -50. However the **open loop gain** of the op-amp is 200. If $R_F = 100\text{k}\Omega$, determine the value of R_S .
6. For the circuit shown in **Fig. 5**, calculate the output voltage (v_o). Assume all op-amps are ideal.

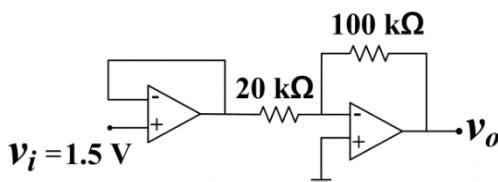


Fig. 5

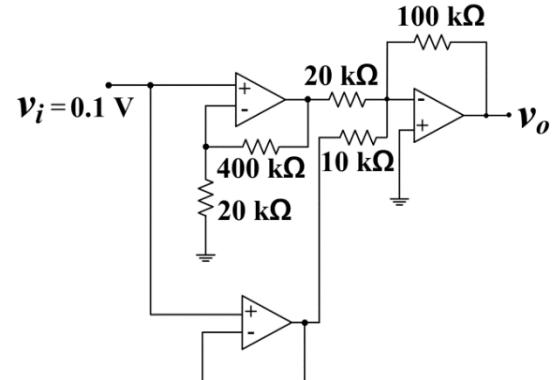


Fig. 6

7. For the circuit shown in **Fig. 6**, calculate the output voltage (v_o). Assume all op-amps are ideal.
8. For the circuit shown in **Fig. 7**, sketch $v_o(t)$ if $v_i(t) = 5 \sin(100\pi t)$. Now, instead of grounding the point 'P' connect it to (a) -3 V and (b) +2 V supply and sketch $v_o(t)$. Assume the op-amp and diode are ideal.



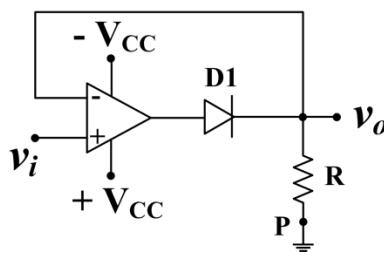


Fig. 7

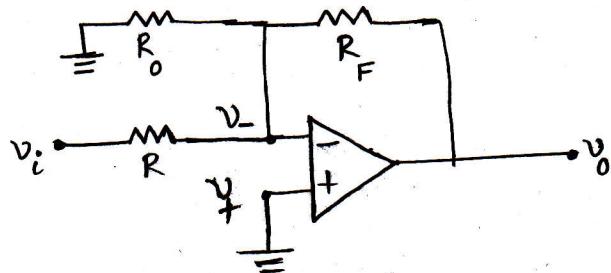

Since the op-amp is ideal $v_+ = v_- = 0$. Hence no current flows through R_o .

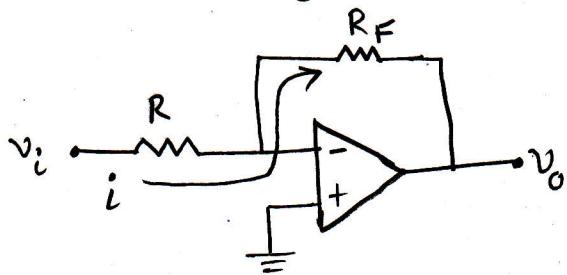
Then we may have the following equivalent circuit



Since same current flows through R and R_F we can write,

$$v_o = - \frac{R_F}{R} v_i$$
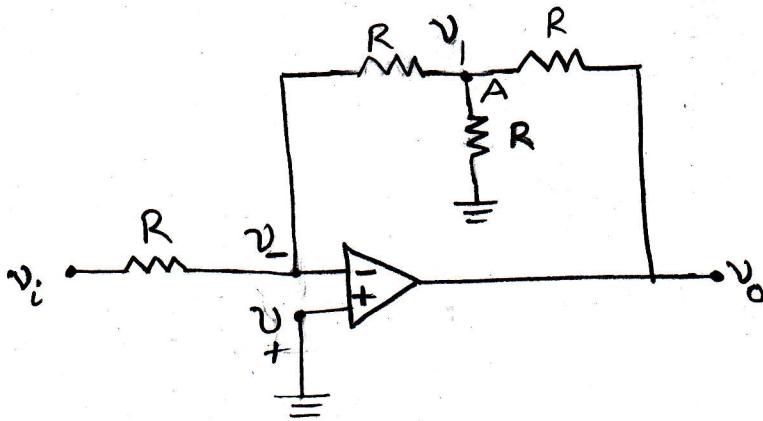
$$\therefore \boxed{v_o = - \frac{R_F}{R} v_i}$$



Since the op-amp is ideal, $v_+ = v_- = 0$. Hence,
 v_+ becomes,

$$v_1 = -\left(\frac{v_i}{R}\right) \cdot R = -v_i \quad \text{--- (1)}$$


Now apply KCL at node 'A'.

$$\frac{v_1}{R} + \frac{v_1}{R} + \frac{v_1 - v_o}{R} = 0 \quad [\because v_- = 0]$$

$$\Rightarrow 3v_1 - v_o = 0$$

$$\Rightarrow -3v_i = v_o \quad [\because \text{From (1)}]$$

$$\therefore \boxed{v_o = -3v_i}$$

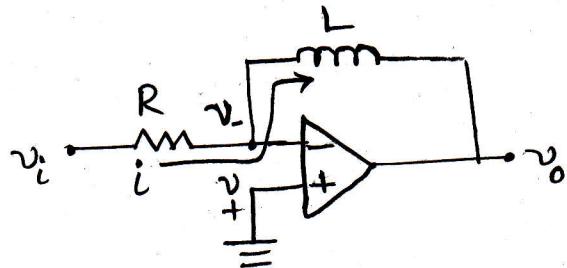


Since the op-amp is ideal $v_+ = v_- = 0$. And same current flows through the resistor, R and inductor, L .

$$i = \frac{v_i}{R}$$


and
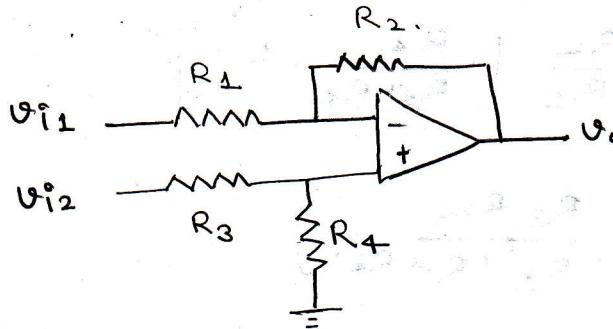
$$\begin{aligned} v_o &= -L \frac{di}{dt} = -L \frac{d}{dt} \left(\frac{v_i}{R} \right) \\ &= -\frac{L}{R} \frac{dv_i}{dt} \\ &= -\frac{L}{R} \cdot 10 \text{ V/s} \end{aligned}$$



i) for determination of A_{cm}. v_{i1} & v_{i2} are tied together to v_i .

So

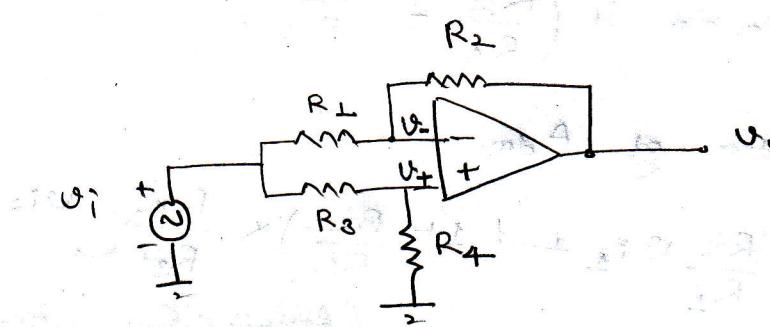

$$\frac{v_i - v_-}{R_2} = \frac{v_- - v_o}{R_2} \Rightarrow \frac{v_i - v_-}{R_2} - \left(\frac{1}{R_1} + \frac{1}{R_3} \right) = -\frac{v_o}{R_2} \quad (i)$$

$$v_+ = v_i \times \frac{R_4}{R_3 + R_4} = v_- \quad (ii)$$

⇒ Substituting v_- from eq. (ii) to eq. (i)

$$\Rightarrow \frac{v_i}{R_1} - v_i \times \frac{R_4}{R_3 + R_4} \times \frac{R_1 + R_2}{R_1 R_2} = -\frac{v_o}{R_2}$$

$$\Rightarrow v_o = v_i \left[-\frac{R_2}{R_1} + \frac{R_4}{R_3 + R_4} \times \left(\frac{R_1 + R_2}{R_1} \right) \right]$$

$$= v_i \left[\frac{R_4}{R_3 + R_4} \times \left(1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} \right]$$

$$\Rightarrow V_o = V_i \left[\frac{R_4}{R_3 + R_4} + \frac{R_2}{R_1} \left(\frac{R_4}{R_3 + R_4} - 1 \right) \right]$$

$$\Rightarrow V_o = V_i \left[\frac{R_4}{R_3 + R_4} - \frac{R_3 R_2}{R_1 (R_3 + R_4)} \right]$$

$$\Rightarrow A_{cm} = \frac{V_o}{V_i} = \frac{R_4}{R_3 + R_4} \left[1 - \frac{R_2}{R_1} \cdot \frac{R_3}{R_4} \right]$$

$$\Rightarrow A_{cm} = 0 \text{ if } \left(\frac{R_2}{R_1} = \frac{R_4}{R_3} \right)$$

ii) Determination of A_{dm} .

$$\Rightarrow V_o = -\frac{R_2}{R_1} V_{i2} + \left(1 + \frac{R_2}{R_1} \right) \times \frac{R_4}{R_3 + R_4} V_{i2}$$

(Applying Superposition principle by considering

$$\Rightarrow \text{So if } \frac{R_2}{R_1} = \frac{R_4}{R_3}, \quad V_{i1} \text{ and } V_{i2} \text{ individually}$$

$$\Rightarrow V_o = -\frac{R_2}{R_1} V_{i2} + \left(1 + \frac{R_4}{R_3} \right) \times \frac{R_4}{R_3 + R_4} V_{i2}$$

$$= -\frac{R_2}{R_1} V_{i2} + \left(\frac{R_3 + R_4}{R_3} \right) \times \frac{R_4}{R_3 + R_4} V_{i2}$$

$$\Rightarrow V_o = -\frac{R_2}{R_1} V_{i2} + \frac{R_4}{R_3} V_{i2} = +\frac{R_2}{R_1} (V_{i2} - V_{i1})$$

for $\left(\frac{R_2}{R_1} = \frac{R_4}{R_3} \right)$

$$\Rightarrow A_{dm} = \frac{V_o}{V_{i2} - V_{i1}} = \frac{R_2}{R_1}$$

$$\therefore \frac{R_4}{R_3} = \frac{100 \text{ k}\Omega}{20 \text{ k}\Omega} = 10 \quad \text{so} \quad \frac{R_2}{R_1} = 9.9 \cdot (1\% \text{ less than } \frac{R_4}{R_3})$$

$$\Rightarrow A_{cm} = \frac{1}{1 + \frac{1}{10}} \times \left(1 - \frac{9.9}{10} \right) = 9.09 \times 10^{-3}$$

$$[\because A_{cm} = \frac{1}{1 + \frac{R_3}{R_4}} \left(1 - \frac{R_2}{R_1} \cdot \frac{R_3}{R_4} \right)]$$

(Determination of Adm)

$$\Rightarrow V_o = -g \cdot g V_{i2} + (1+g \cdot g) \times \frac{1}{1 + \frac{1}{10}} \times V_{i2}$$

$$V_o = -g \cdot g V_{i2} + 10 \cdot g \times \frac{10}{11} V_{i2}$$

$$V_o = -g \cdot g V_{i2} + g \cdot g \cdot 9 V_{i2}$$

$$V_o \approx g \cdot g (V_{i2} - V_{i1})$$


$$\Rightarrow Adm \approx g \cdot g$$

$$CMRR = 20 \log_{10} \left(\frac{Adm}{Acm} \right)$$

$$= 60.7 \text{ dB}$$

$$V_o = 2V_{i1} + 3V_{i2} - 4(V_{i3} + 5V_{i4})$$

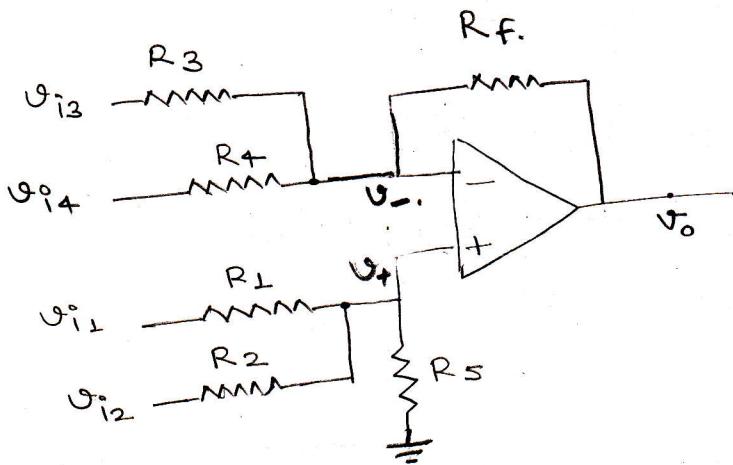For implementation of V_o from given set of inputs ($V_{i1}, V_{i2}, V_{i3}, V_{i4}$)
 Inverting & non-inverting configurations of OPAMPS are required



Applying superposition theorem,

$$\frac{V_o}{V_{i3}} = -\frac{R_F}{R_3} = -4 \text{ with } V_{i1} = V_{i2} = V_{i4} = 0 \text{, and}$$

$$\frac{V_o}{V_{i4}} = -\frac{R_F}{R_4} = -20 \text{ with } V_{i1} = V_{i2} = V_{i3} = 0$$

$$\text{Thus, } \frac{R_F}{R_3} = 4 \text{ and } \frac{R_F}{R_4} = 20$$

Choosing $R_4 = 1 \text{ K}$, will lead to $R_F = 20 \text{ K}$ and $R_3 = 5 \text{ K}$.

Now, considering V_{i1} with $V_{i2} = V_{i3} = V_{i4} = 0$,

$$V_+ = V_{i1} \times \frac{R_2 || R_5}{R_1 + R_2 || R_5} = V_{i1} \times \frac{(R_2 R_5) / (R_2 + R_5)}{R_1 + R_2 R_5 / R_2 + R_5}$$

$$= V_{i1} \times \frac{R_2 R_5}{R_1 R_2 + R_1 R_5 + R_2 R_5}$$

$$= V_{i1} \times \frac{R_2 R_5}{R_1 R_2 + R_1 R_5 + R_2 R_5}$$

$$R'' = R_1 || R_2 || R_5 \quad \dots \text{---(i)}$$

$$\text{Now, } \frac{V_o}{V_+} = 1 + \frac{R_F}{R_3 || R_4} = 1 + \frac{20 \times 6}{8 \times 1} = 25$$

$$\Rightarrow \frac{V_o \times R_1}{V_{i1} \times R''} = 25 \Rightarrow \frac{V_o}{V_{i1}} = \frac{25 \times R''}{R_1}$$

$$\therefore \frac{V_0}{V_{i1}} = 2 \Rightarrow \frac{25 \times R''}{R_1} = 2$$

$$\Rightarrow \frac{R''}{R_1} = \frac{2}{25} = 0.08$$

$$\Rightarrow R_1 = 12.5 R'' \quad \text{--- (ii)} \quad \frac{R''}{R_2} = 0.08$$

considering V_{i2} , with $V_{i1} = V_{i3} = V_{iu} = 0$

we obtain,

$$V_+ = V_{i2} \times \frac{R_1 \parallel R_S}{R_2 + R_1 \parallel R_S} = V_{i2} \times \frac{R''}{R_2}$$

$$\Rightarrow V_0 = \left(1 + \frac{R_F}{R_3 \parallel R_y} \right) \times \frac{R''}{R_2} \times V_{i2} \quad \therefore \frac{V_0}{V_{i2}} = 3.$$

$$\Rightarrow \left(1 + \frac{20K \times 6K}{5K \parallel 3} \right) \times \frac{R''}{R_2} = 3 \quad \Rightarrow \frac{R''}{R_2} = 0.12$$

$$\Rightarrow 25 \times \frac{R''}{R_2} = 3 \Rightarrow \frac{R''}{R_2} = \frac{3}{25} = 0.12$$

$$\Rightarrow R_2 = 8.33 R'' \quad \text{--- (iii)}$$

$$\text{from eq. (i) } 2(\text{ii}) \quad R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{12.5 R'' \times 8.33 R''}{12.5 R'' + 8.33 R''}$$

$$\Rightarrow R_1 \parallel R_2 = 5 R'' \quad \therefore \text{from eq. (i) } R'' = R_1 \parallel R_2 \parallel R_S.$$

$$\Rightarrow R'' = 5 R'' \parallel R_S \Rightarrow R'' = \frac{5 R'' R_S}{5 R'' + R_S} \Rightarrow 5 R'' + R_S = 5 R_S$$

$$\Rightarrow R_S = 1.25 R''. \quad \text{--- (iv)}$$

\therefore All the resistor have to be in range of $1K\Omega - 100K\Omega$

\therefore from eq. (ii) & (iii) R_1 is larger than R_2 .

So choose $R_L = 100 \text{ k}\Omega$

∴ from eq(iii)


$$\Rightarrow R'' = \frac{R_L}{12.5} = 8 \text{ k}\Omega$$

from eq. (iii)

$$\Rightarrow R_2 = 66.64 \text{ k}\Omega$$

∴ from eq. (iv)
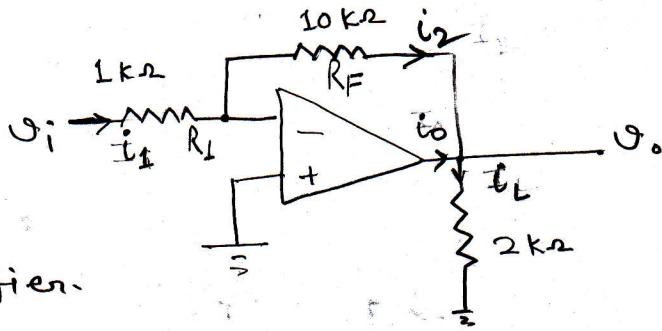
$$\Rightarrow R_S = 1.25 \times 8 \text{ k}\Omega = 10 \text{ k}\Omega$$



∴ This is an inverting amplifier & for an inverting amplifier.

$$\Rightarrow \frac{V_o}{V_i} = -\frac{R_F}{R_1} = -\frac{10K}{1K} = -10.$$

a) $V_o = -10V$ if $V_i = +1V$

$$i_1 = \frac{V_i}{R_1} = \frac{1}{1K} = 1mA.$$

$$\Rightarrow i_2 = i_{11} = 1mA$$

$$\Rightarrow i_L = \frac{V_o}{2K} = -\frac{10}{2K} = -5mA$$

$$\Rightarrow i_o + i_2 = i_L \Rightarrow i_o = -5mA - 1mA = -6mA$$

∴ Op-Amp is sinking current.

b) if $V_i = -1V$ $V_o = 10V$


$$\therefore i_1 = \frac{V_i}{R_1} = -\frac{1}{1K} = -1mA.$$

$$\Rightarrow i_2 = i_1 = -1mA.$$

$$\Rightarrow i_L = \frac{V_o}{2K} = \frac{10}{2K} = 5mA.$$

$$\Rightarrow i_o = i_L - i_2 = 5mA + 1mA = 6mA.$$

∴ Op-Amp is supplying current.

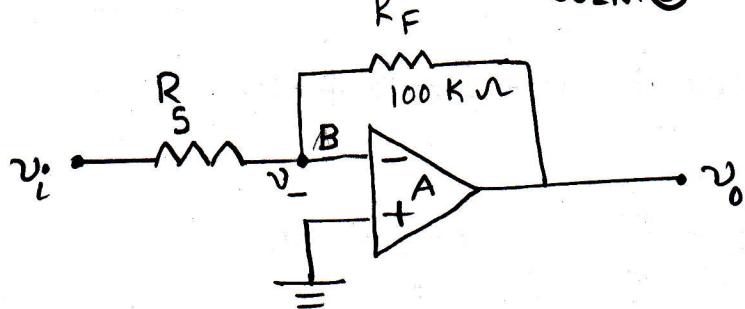

given

$$\text{open loop gain, } A = 200$$

$$\text{desired gain, } \frac{v_o}{v_i} = -50 \Rightarrow v_o = -50 v_i \quad \text{--- ①}$$

But from the figure,

$$A = -\frac{v_o}{(v_- - 0)} = 200 \Rightarrow v_o = -200 v_- \quad \text{--- ②}$$

Applying KCL at node "B", we get

$$\frac{v_- - v_i}{R_s} + \frac{v_- - v_o}{R_F} = 0$$

$$\Rightarrow v_- \left(\frac{1}{R_s} + \frac{1}{R_F} \right) = \frac{v_o}{R_F} + \frac{v_i}{R_s}$$

$$\begin{aligned} \Rightarrow v_- (R_s + R_F) &= v_o R_s + v_i R_F \\ &= v_o R_s - \frac{v_o}{50} R_F \quad [\because \text{From ①}] \end{aligned}$$

$$\begin{aligned} \Rightarrow v_- (R_s + R_F) &= \left(R_s - \frac{R_F}{50} \right) v_o \\ &= \left(R_s - \frac{R_F}{50} \right) \times (-200 v_-) \quad [\because \text{From ②}] \end{aligned}$$

$$\Rightarrow R_s + 100 \text{ k} = -200 R_s + \left(\frac{200}{50} \times 100 \text{ k} \right)$$


$$\Rightarrow R_s + 100 \text{ k} = -200 R_s + 400 \text{ k}$$

$$\Rightarrow 200 R_s + R_s = -100 \text{ k} + 400 \text{ k}$$

$$\Rightarrow 201 R_s = 300 \text{ k}$$

$$\Rightarrow R_s = \frac{300 \text{ k}}{201} = 1.492 \text{ kN}$$

$$\therefore R_s = 1.492 \text{ kN}$$

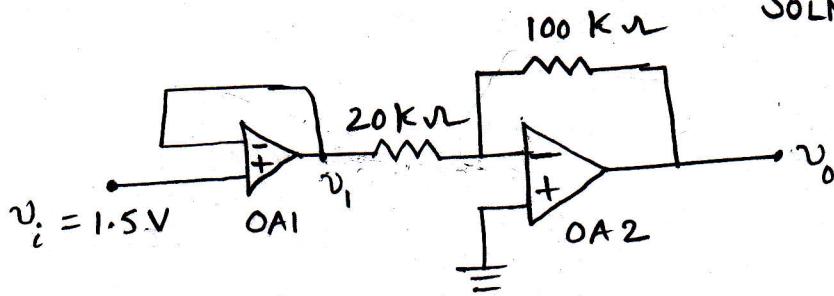

if both the op-amps OA1 and OA2 are assumed to be ideal,

then


$$v_1 = v_i = 1.5 \text{ V}$$

Op-amps are ideal, therefore loading of second op-amp by first op-amp will be minimum. (Input impedance: high
Output impedance: very low)

we can write that,

$$\begin{aligned} v_o &= - \frac{100 \text{ k}}{20 \text{ k}} \times v_i \\ &= - 5 \times 1.5 \text{ V} = - 7.5 \text{ V} \end{aligned}$$

$$\therefore v_o = - 7.5 \text{ V}$$

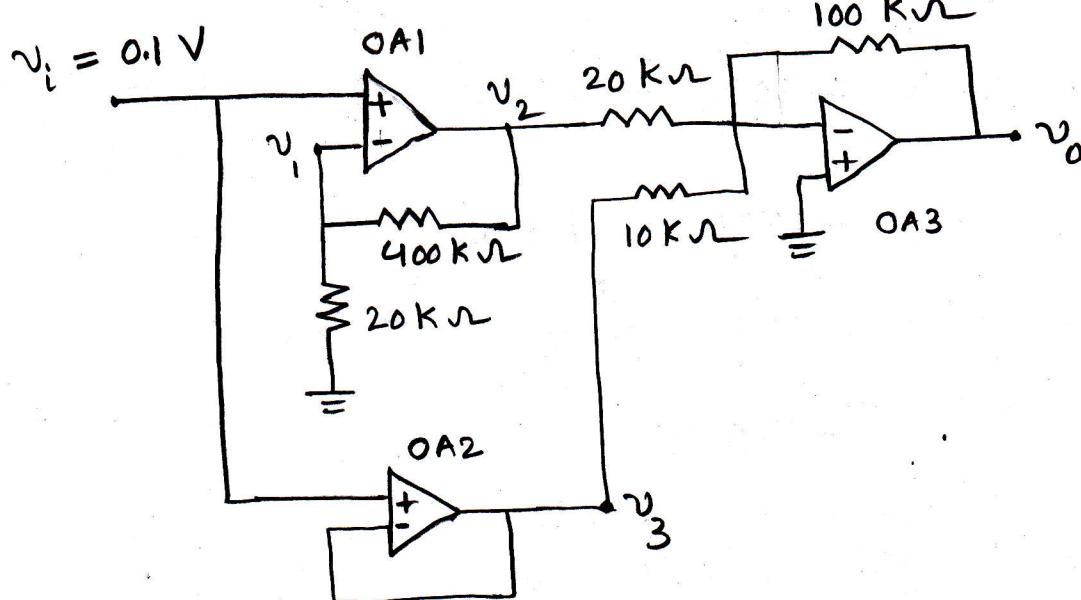

If all the op-amps depicted in the figure, are assumed to be ideal, then


$$v_1 = v_3 = v_i = 0.1 \text{ V} \quad \text{--- (1)}$$

and

$$\begin{aligned} v_2 &= v_i \left[1 + \frac{400 \text{ K}}{20 \text{ K}} \right] = v_i [1 + 20] \\ &= 21 v_i \quad [\because \text{From (1)}] \end{aligned}$$

$$\Rightarrow v_2 = 21 v_i \quad \text{--- (2)}$$

Now the op-amp OA3 becomes,

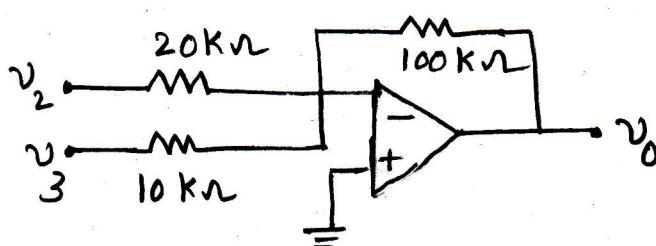

$$\begin{aligned} v_o &= -\left(\frac{100 \text{ K}}{10 \text{ K}}\right)v_3 - \left(\frac{100 \text{ K}}{20 \text{ K}}\right)v_2 \\ &= -10v_3 - 5v_2 \end{aligned}$$

$$\Rightarrow v_o = -10v_i - 5(21v_i) \quad [\because \text{From } ① \text{ & } ②]$$



$$= -10v_i - 105v_i$$

$$= -115 \times 0.1 \text{ V} \quad [\because v_i = 0.1 \text{ V}]$$

given

$$= -11.5 \text{ V}$$

$$v_o = -11.5 \text{ V}$$

 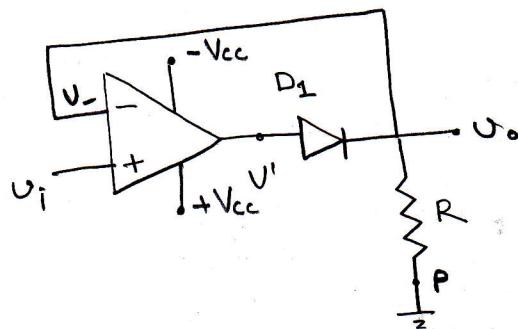

→ consider diode D_1 is not conducting (cut-off).
Then there will be no current in R .

$$\therefore V_o = V_- = 0$$


As $V_i > 0 \text{ V}$ (+ve half cycle).

$$\text{then } V_+ > V_- \Rightarrow V' = +V_{cc}$$

so D_1 will start conducting & equivalent circuit will become:-

∴ This is voltage follower.

$$V_o = V_i$$


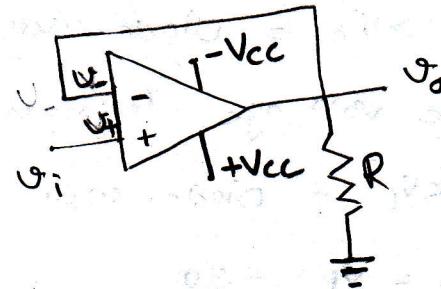


→ During -ve half cycle.

$$V' = \text{output of op-amp} = -V_{cc}$$

so diode will go in cut-off mode.

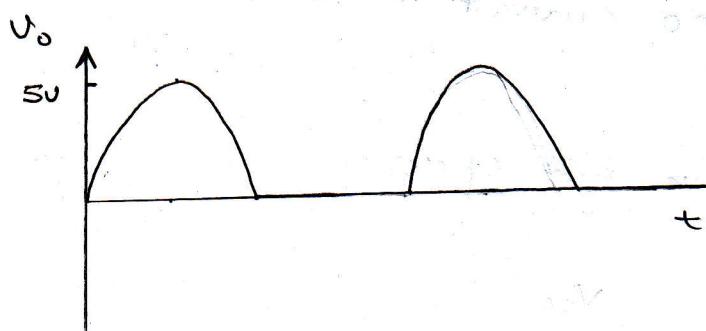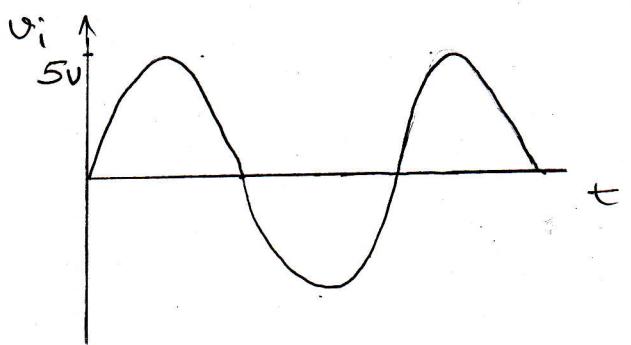so no current will flow through R . so $V_o = 0$.




a) if $V_p = -3V$.

when $V_i > V_p = -3V$ = Diode will conduct & circuit will

become voltage follower. So, $V_o = V_i$

when $V_i < V_p = -3V$ = Diode will be in cut-off mode.

so $V_o = V_p = -3V$.

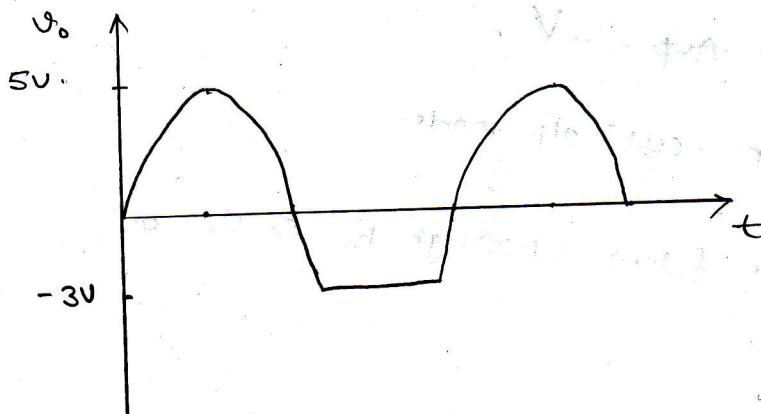

b) if $V_P = +2V$.

when $V_i > V_P = \text{Diode will conduct}$

$$\& V_o = V_i$$

$V_i < V_P = \text{Diode will be in cut-off and } V_o = 2V$

