
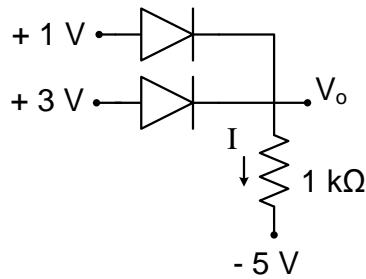


8th September, 2016**Home Assignment – 6**

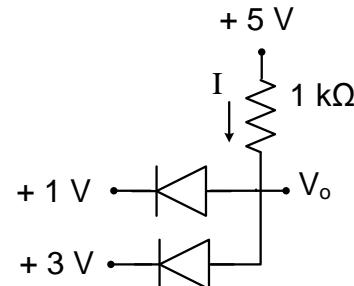
1. For the circuit shown in **Fig. 1**, using ideal diodes, find the voltage (V_o) and current (I) indicated.




(a)



(b)

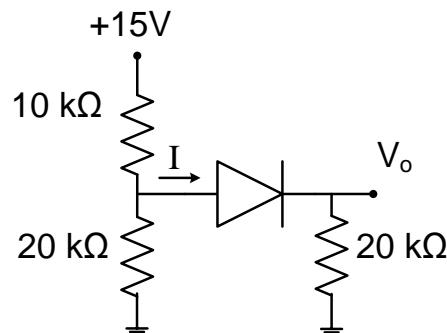



(c)

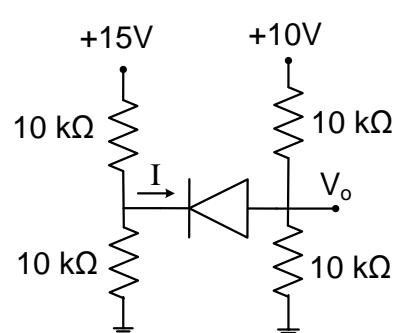



(d)

Fig. 1

2. For the circuit shown in **Fig. 2**, sketch the output voltage waveform with time. When diode conducts, voltage drop is 0.7 V and forward resistance is 50 Ω. In OFF state diode is open circuit. Assume $V_i = 15 \sin(\omega t)$ V.

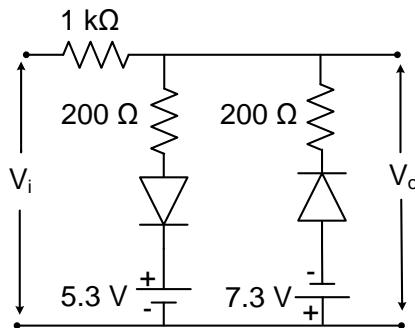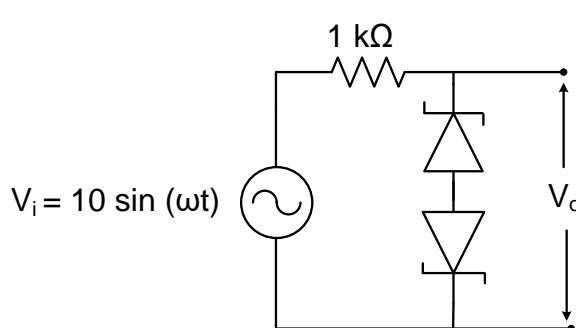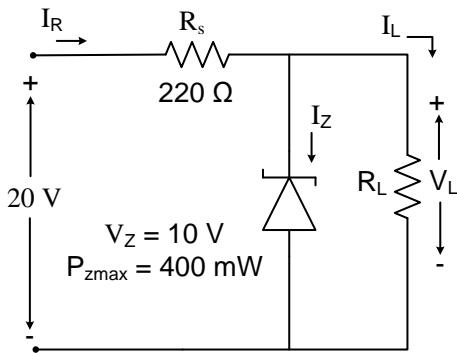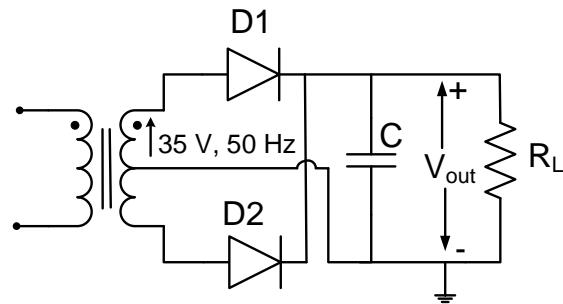
**Fig. 2****Fig. 3**

3. The Zener diodes used in **Fig. 3** have the following characteristics: Forward drop = 0.7 V; Zener voltage = - 7 V; R_f (Forward Resistance) = 20 Ω ; R_z (Resistance in Zener region) = 10 Ω . Sketch the output waveform V_o with time.
4. (a) Determine V_L , I_L , I_Z and I_R for the voltage regulator network shown in **Fig. 4** if $R_L = 180 \Omega$.
- (b) Repeat part (a) if $R_L = 470 \Omega$.
- (c) Determine the value of R_L that will establish maximum power conditions in the Zener diodes.
- (d) Determine the minimum value of R_L to ensure that the Zener diode is "ON" state.

**Fig. 4****Fig. 5**

5. A Full Wave Rectifier is shown in **Fig. 5**. The center tapped transformer voltage is 35 V rms, 50 Hz. A 160 μF capacitor is connected in the output to filter out the load voltage ripple. A load of 250 Ω is connected in parallel with filter capacitor. Assume that the cut-off voltage of diode is 0.7 V and forward biased resistance is zero.
- (a) Plot the output voltage V_o and diode current i_D at steady state.
- (b) Calculate the ripple voltage and maximum diode current.
- (c) Calculate the peak inverse voltage.
6. A Full Wave Bridge Rectifier is used to design a dc power supply that provides an average dc output voltage of 15 V on which a maximum of ± 1 V ripple is allowed. The rectifier feeds a load of 150 Ω . The rectifier is fed from the line voltage (120 V rms, 60 Hz) through a transformer. The diodes available have 0.7 V drop when conducting.
- (a) Specify the **rms** voltage that must appear across the transformer secondary.
- (b) Find the required value of the filter capacitor.
- (c) Find the **PIV rating** of the diode.


(a)

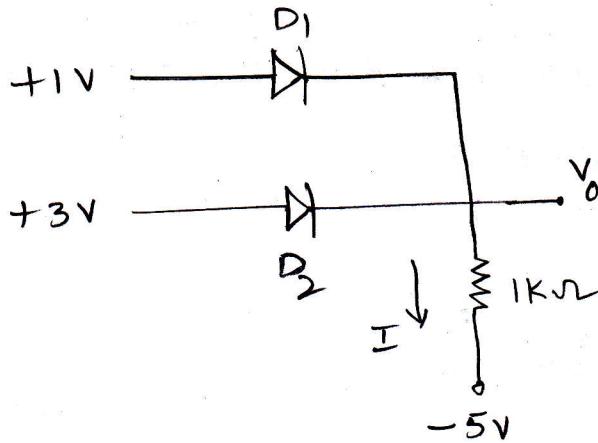

case (i) :-

Assume both D_1 and D_2 are ON.

Then the circuit reduces to,

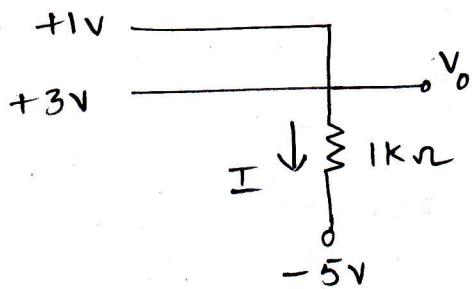


It can be seen that

the case is contradicting. This implies D_1 & D_2 cannot be 'on' simultaneously. Hence, the assumption is false.

case (ii) :-

Assume D_1 is ON, and D_2 is OFF.

Then the circuit reduces to,

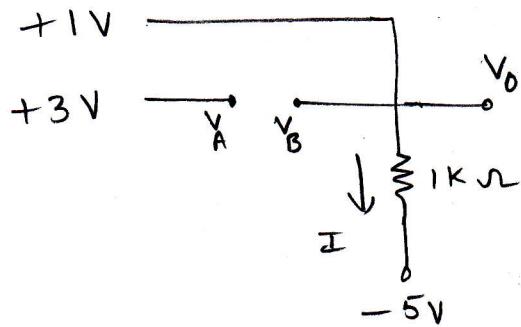


$$\text{Here, } V_0 = +1V = V_B$$

But $V_A = 3V \gg V_B \Rightarrow D_2$ must be ON.

Hence, our assumption is False.

case (iii) :-

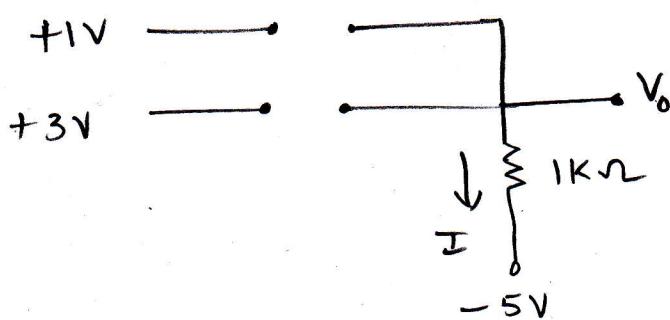
Assume both D_1 and D_2 are OFF.

Here $V_0 = -5V \Rightarrow$ this implies D_1 and D_2 must be ON [as in case (i)]. Again the assumption fails.

case (iv):-

Assume D_1 is OFF and D_2 is ON.

Then the circuit reduces to,

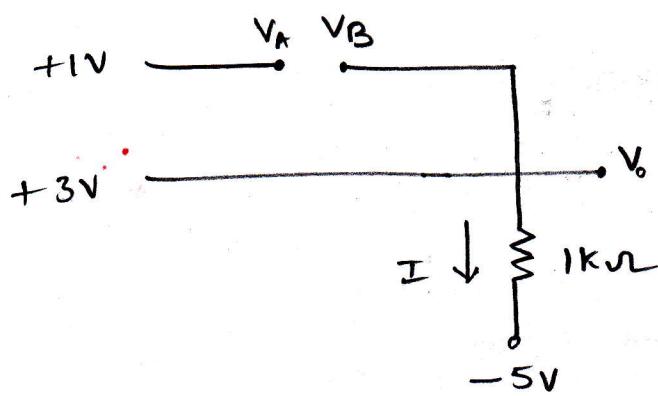



Here, $V_o = +3V \Rightarrow$ which implies D_1 is OFF $[V_B > V_A]$

Hence the assumption is true.

$$\Rightarrow I = \frac{V_o - (-5V)}{1k\Omega} = \frac{3V - (-5V)}{1k\Omega} = 8mA$$

$$\boxed{\begin{aligned} V_o &= 3V \\ I &= 8mA \end{aligned}}$$

(b)

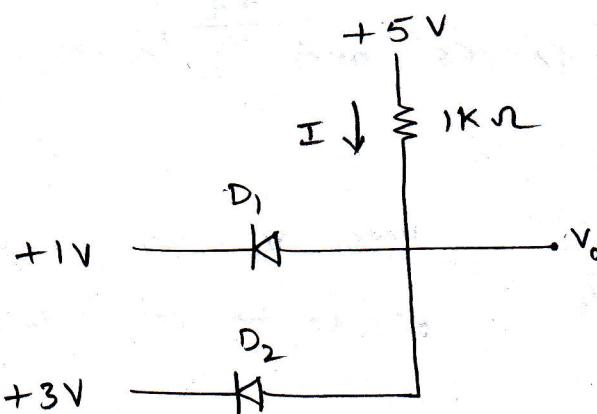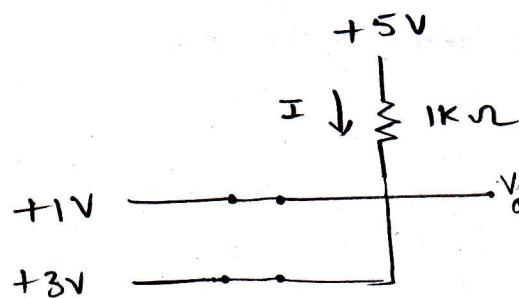
case (i) :-Assume both D_1 & D_2 are 'on'

It can be seen that

the case is contradicting

and the two diodes cannot be 'on' simultaneously.

Hence, the assumption is false.

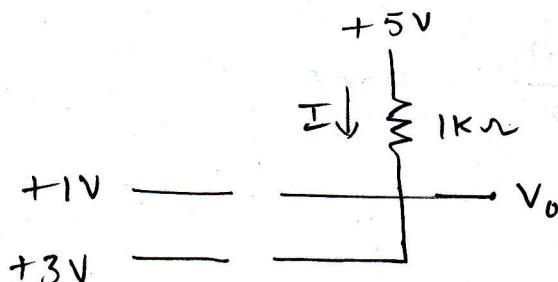case (ii) :-Assume both D_1 & D_2 are OFF.


Then $V_o = 5V$, which forces
 D_1 and D_2 to be forward biased;
which again is a malcondition.

So, the assumption fails.

case (iii):-

Assume D_1 is OFF and D_2 is ON.

P-4

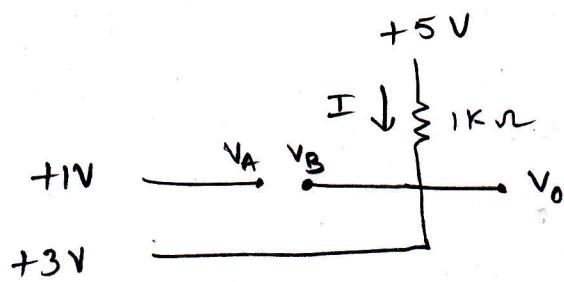


Here, $V_o = 3V$ which forces D_1 to be ON. $[V_B > V_A]$

Hence, the assumption is incorrect.

case (iv):-

Assume D_1 is ON and D_2 is OFF.

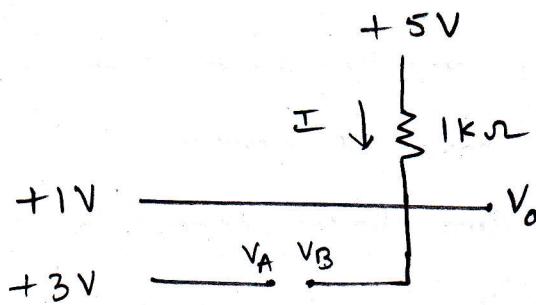

Here, $V_o = 1V$ which forces D_2 to be OFF. $[V_B < V_A]$

So the assumption is correct.


Now,

$$I = \frac{5 - V_o}{1k} = \frac{5 - 1}{1k} = 4mA$$

$V_o = 1V$
$I = 4mA$

P-5

(c)

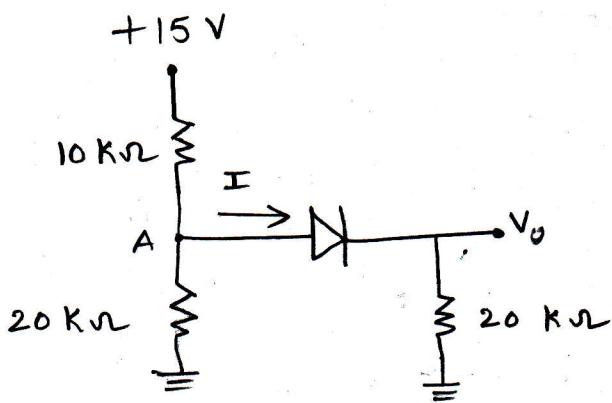

Assume the diode is OFF. Then,

$$\begin{aligned}
 & +15V \\
 & \text{---} \\
 & | \quad | \\
 & 10k\Omega \quad V_A \\
 & | \quad | \\
 & 20k\Omega \quad \text{---} \\
 & \quad \quad \quad V_o \quad | \\
 & \quad \quad \quad 20k\Omega \quad | \\
 & \quad \quad \quad \text{---}
 \end{aligned}$$

$$\begin{aligned}
 V_A &= 15 \times \frac{20k}{20k+10k} \\
 &= 15 \times \frac{20}{30} = 10V \\
 \text{and } V_o &= 0
 \end{aligned}$$

Since $V_A > V_o \Rightarrow$ Diode is Forward Biased.

So the assumption is False.

when the diode is ON,

$$\begin{aligned}
 & +15V \\
 & \text{---} \\
 & | \quad | \\
 & 10k\Omega \quad I \\
 & | \quad | \\
 & 20k\Omega \quad \text{---} \\
 & \quad \quad \quad V_o \quad | \\
 & \quad \quad \quad 20k\Omega \quad | \\
 & \quad \quad \quad \text{---}
 \end{aligned}$$


$$\begin{aligned}
 V_o &= 15 \times \frac{(20k \parallel 20k)}{10k + [20k \parallel 20k]} \\
 &= 15 \times \frac{10k}{20k} = 7.5V
 \end{aligned}$$

and,


$$I = \frac{V_o}{20k} = \frac{7.5}{20k\Omega} = 0.375mA$$

$V_o = 7.5V$
$I = 0.375mA$

(d)

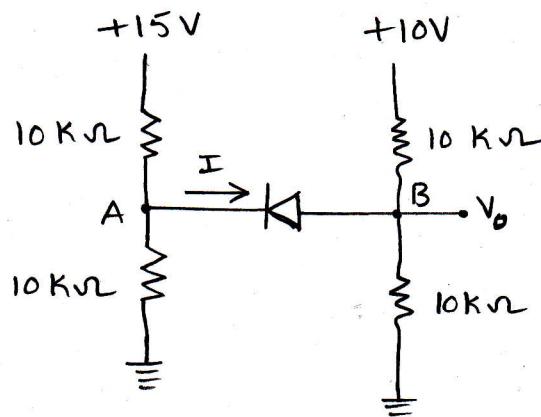

Assume that, the diode is OFF. Then,

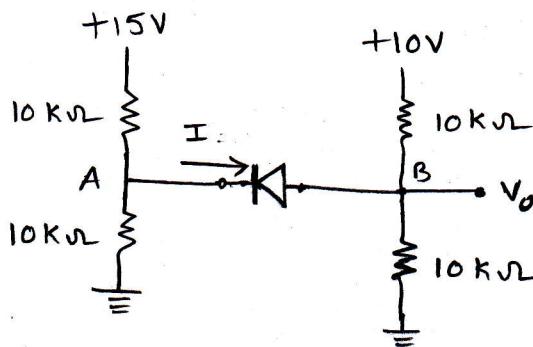

Now,

$$V_A = 15 \times \frac{10k}{10k+10k} = \frac{15}{2} = 7.5V$$


$$V_B = 10 \times \frac{10k}{10k+10k} = 10 \times \frac{1}{2} = 5V \Rightarrow V_B = 5V$$

Since $V_A > V_B$ i.e., Diode is reverse biased i.e., OFF.

So, the assumption is correct and as the diode is reverse-biased,
no current will flow through it i.e., $I=0$,

$$\therefore V_o = V_B = 5V$$
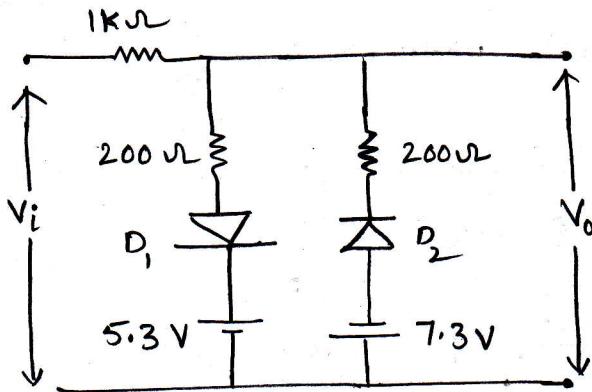
$$\boxed{\begin{aligned} V_o &= 5V \\ I &= 0A \end{aligned}}$$




$$V_i = 15 \sin(\omega t)$$

→ During +ve half cycle of V_i ,

D_1 conducts and D_2 gets OFF.

Then the circuit reduces to,

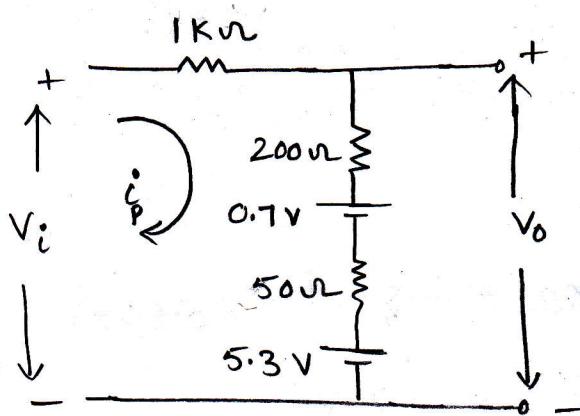

$$i_p = \frac{V_i - 0.7 - 5.3}{1000 + 200 + 50} = \frac{V_i - 6}{1250}$$

for $V_i < 6V \Rightarrow V_0 = V_i$ (D_1 will conduct when $V_i > 6V$)


$$i_{p\max} = \frac{V_{i,\max} - 6}{1250} = \frac{15 - 6}{1250} = \frac{9}{1250} = 7.2 \text{ mA}$$

$$V_{0,\max} = 15 - (1k \times 7.2 \times 10^{-3}) = 7.8 \text{ V}$$

→ During -ve half cycle of V_i

D_2 conducts and D_1 gets OFF.

Then the circuit reduces to,

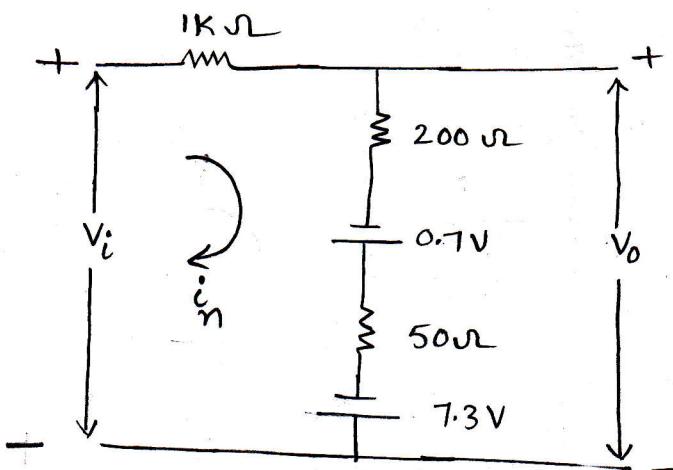


$$i = \frac{V_i + 7.3 + 0.7}{1000 + 200 + 50} = \frac{V_i + 8}{1250} \Rightarrow \text{For } -8V \leq V_i \leq 0V \quad V_o = V_i$$

when $V_i = -15V \Rightarrow i_{n,\min} = \frac{-15 + 8}{1250} = -\frac{7}{1250}$


$$= -5.6 \text{ mA}$$

$$\therefore V_{o,\min} = -15 - i_{n,\min} \cdot 1k\Omega = -15 + [1k \times 5.6 \text{ mA}] \\ = (-15 + 5.6)V = -9.4V$$

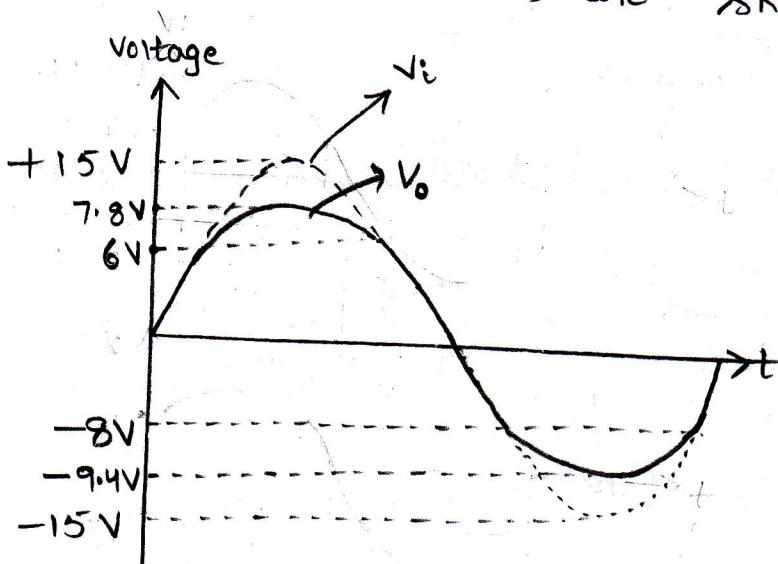The desired waveforms are sketched below.



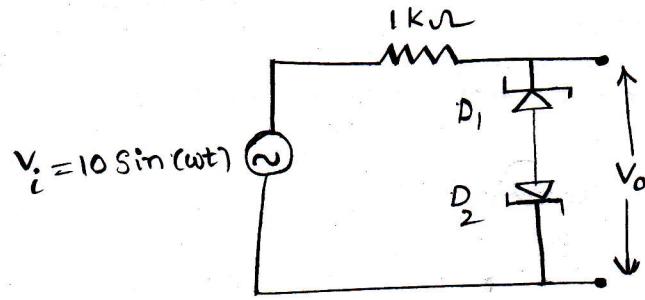FOR $-8V \leq V_i \leq 6V$
 D_1 and D_2 are OFF
 $\Rightarrow V_o = V_i$



given


$$V_f = 0.7 \text{ V} ; V_z = -7 \text{ V} ; R_f = 20 \Omega$$

$$\text{and } R_z = 10 \Omega$$

→ During +ve half cycle,

D_1 acts as a zener and D_2 acts as a normal diode

The circuit reduces to,

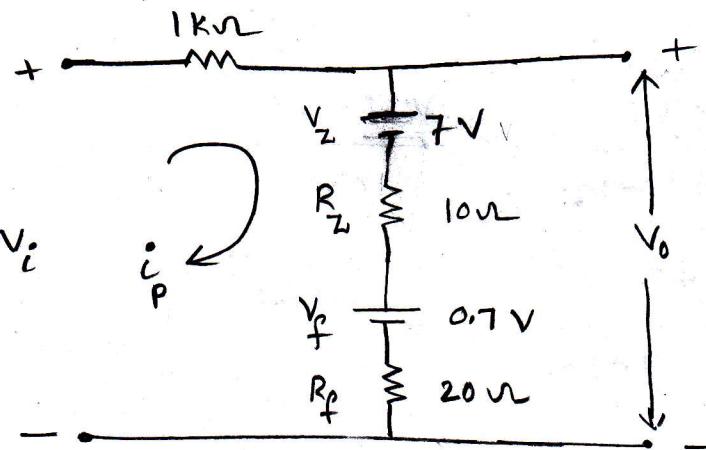

$$\text{when } V_i < (7 + 0.7 = 7.7 \text{ V}) \Rightarrow V_o = V_i$$

$$\text{when } V_i \geq 7.7 \text{ V},$$

$$i_p = \frac{V_i - 0.7 - 7}{1000 + 10 + 20} = \frac{V_i - 7.7}{1030}$$


$$\Rightarrow i_{p,\max} = \frac{V_{i,\max} - 7.7}{1030} = \frac{10 - 7.7}{1030} = 2.23 \text{ mA}$$

$$\therefore V_{o,\max} = V_{i,\max} - [1k \times i_{p,\max}] = 10 - 2.23 = 7.77 \text{ V}$$

During -ve half cycle,

D_1 acts as a normal diode

and D_2 acts as a zener

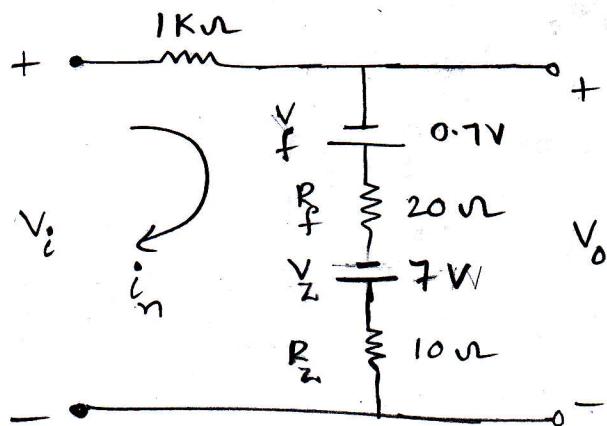


$$\text{For } -7.7V < V_i < 0 ; V_o = V_i$$

for $V_i < -7.7V$,

$$i_n = \frac{V_i + 7.7}{1000 + 20 + 10} = \frac{V_i + 7.7}{1030}$$

$$\Rightarrow i_{n,\min} = \frac{V_{i,\min} + 7.7}{1030} = \frac{-10 + 7.7}{1030} = -2.23 \text{ mA.}$$
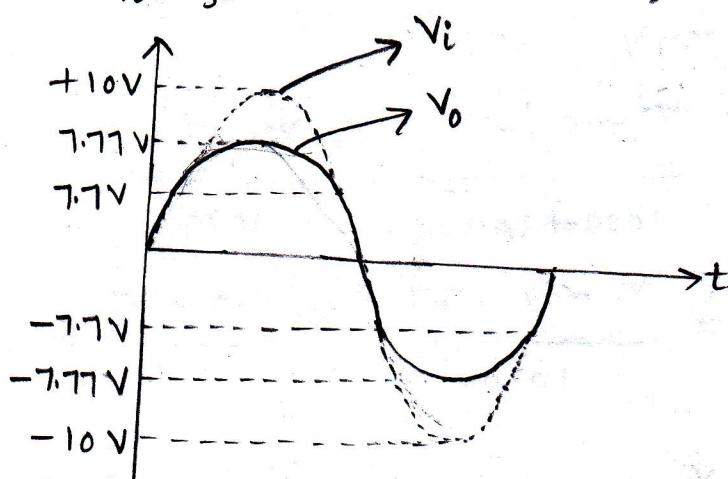
$$V_{o,\min} = -10 - i_{n,\max} \cdot 1k\Omega = -10 + [2.23 \times 10^{-3} \times 1 \times 10^3] \\ = (-10 + 2.23)V = -7.77V$$



a) ∵ In the absence of Zener diode.

$$V_L = 20 \times \frac{R_L}{R_L + R_s} = 20 \times \frac{180}{180 + 220}$$

$$= 9V.$$

$$\therefore V_z = 10V \quad \Rightarrow \quad V_L < V_z.$$

so Zener diode is not conducting.

$$\therefore I_L = \frac{20}{R_s + R_L} = \frac{20}{180 + 220} = 50 \text{ mA.}$$

$$\Rightarrow I_L = I_R = 50 \text{ mA.} \quad \text{so } I_z = 0 \text{ A.}$$

$$V_L = 9V$$

$$b) \because R_L = 470\Omega.$$

so in absence of Zener diode

$$V_L = 20 \times \frac{R_L}{R_L + R_s} = 20 \times \frac{470}{470 + 220} = 13.62 \text{ V.}$$

∴ $V_L > V_z$, so Zener diode is ON.

$$\therefore V_L = 10V. \quad I_L = \frac{10}{470} = 21.27 \text{ mA.}$$

$$\Rightarrow I_R = \frac{20 - 10}{220} = 45.45 \text{ mA.}$$

$$\Rightarrow I_z = I_R - I_L = 24.18 \text{ mA.}$$

$$c) \because P_{z\max} = 400 \text{ mW} = V_z \cdot I_{z\max}$$

$$\Rightarrow I_{z\max} = \frac{400 \times 10^{-3}}{10} = 40 \text{ mA.}$$

$$\Rightarrow I_{L\min} = I_R - I_{z\max} = \frac{45.45 \text{ mA} - 40 \text{ mA}}{10} = 5.45 \text{ mA}$$

$$\therefore R_L = \frac{V_L}{I_{L\min}} = \frac{10}{5.45 \times 10^{-3}} = 1.82 \text{ k}\Omega$$

a) Minm. voltage required for the Zener to be ON = 10V.
 min. $V_L = 10V$

$$\Rightarrow 10 = 20 \times \frac{R_L}{R_L + 220}$$

$$\Rightarrow R_L + 220 = 2R_L$$

$$\Rightarrow R_L = 220 \Omega$$


SOLN. ⑤

P-13


$$\therefore V_i = 35\sqrt{2} \sin \omega t$$

$$C = 160 \mu F$$

$$R_L = 250 \Omega$$

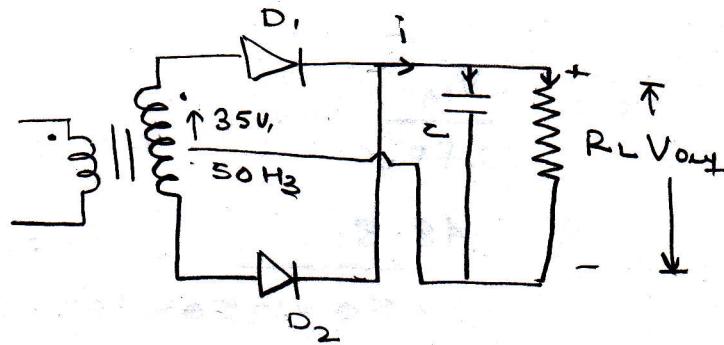

a)

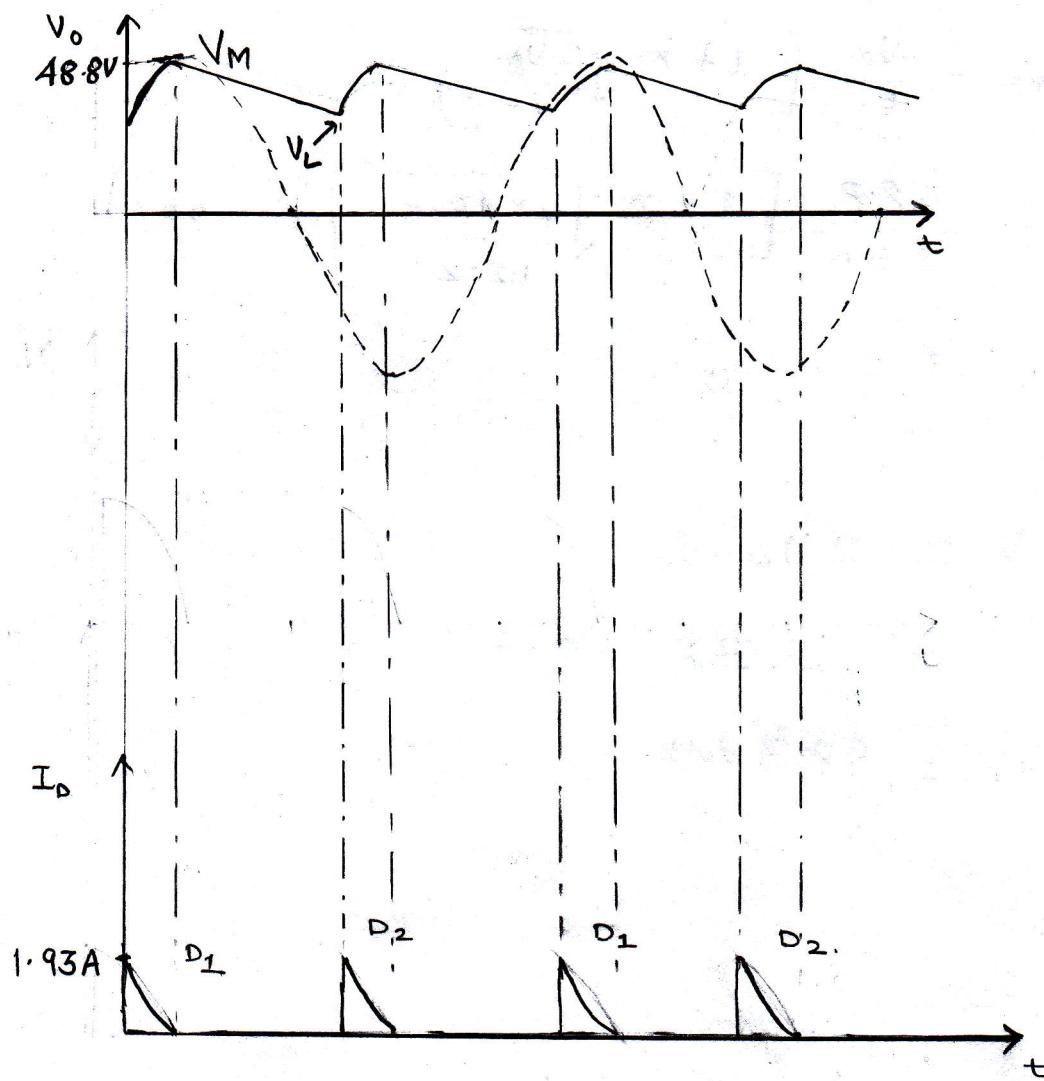

b) $V_m = 35\sqrt{2} V$

$$V_M = 35\sqrt{2} - 0.7 = 48.8 V$$

$(V_m \sin \omega t) \rightarrow$ Input voltage to diode

$$V_M \rightarrow \text{Maximum voltage at output}$$

$$V_M = V_m - V_r$$

$$\Rightarrow V_r = \frac{V_m}{2fR_L C}$$

$$= \frac{48.8}{2 \times 50 \times 250 \times 160 \times 10^{-6}}$$

$$= 12.2 \text{ Volt}$$


$$\Rightarrow I_{D, \text{max}} = \frac{V_m}{R_L} \left[1 + \pi \sqrt{\frac{2V_m}{V_r}} \right]$$

$$= \frac{48.8}{250} \left[1 + \pi \sqrt{\frac{2 \times 48.8}{12.2}} \right] = 1.93 \text{ A}$$


$$\therefore PIV = 2V_m - V_\gamma$$

$$= (2 \times 35\sqrt{2}) - 0.7$$

$$= 98.3 \text{ Volt.}$$

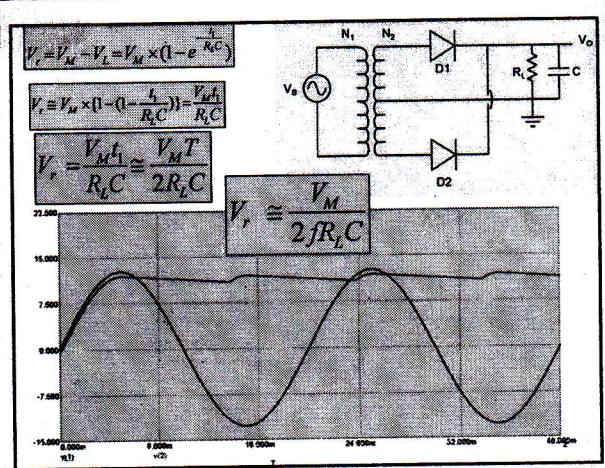

Peak Inverse Voltage

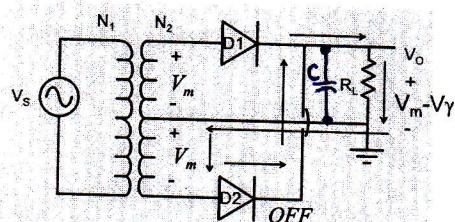


$$V_m + V_D + V_m - V_r = 0$$

$$V_D = -(2V_m - V_r) \quad PIV = 2V_m - V_r$$

$$V_p = 120 \text{ Vms.}$$

$$V_o = 15 \pm 1\text{V.}$$
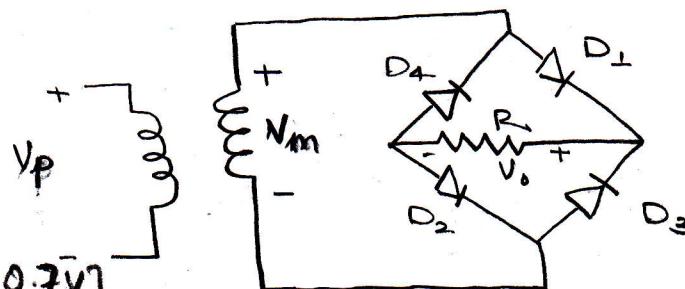
$$\therefore V_m = V_o + 2V_8 \quad [V_8 = 0.7\text{V}] \\ = 16 + 1.4 = 17.4 \text{V}$$



a) $\Rightarrow V_s = \frac{V_m}{\sqrt{2}} = \frac{17.4}{\sqrt{2}} = 12.3 \text{V.} \quad [\text{rms Voltage appearing across transformer secondary}]$

b) $V_r = \frac{V_m}{2 f C R_L} \quad \Rightarrow \quad 2 = \frac{16}{2 \times 60 \times C \times 150} \quad [V_m = 16 \text{V and } V_r = 2 \text{V}]$

$$\Rightarrow C = 444.44 \mu\text{F}$$

c) for the diodes,

$$\begin{aligned} PIV &= V_o + V_8 \\ &= (16 + 0.7)\text{V} \\ &= 16.7 \text{V.} \end{aligned}$$

