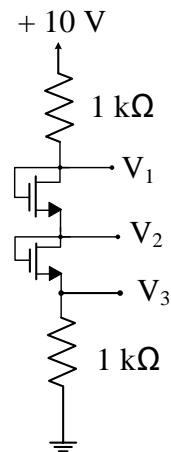



29th September, 2016**Home Assignment – 8**

1. For the circuit shown in **Fig. 1**, determine the **labeled node voltages**. The NMOS transistors are identical having $V_t = 1$ V and $k'_n \frac{W}{L} = 2$ mA/V².


**Fig. 1**

2. A Common Source amplifier is shown in **Fig. 2**.


- (a) Verify that biasing of NMOS is proper ($V_t = 1$ V and $k'_n \frac{W}{L} = 2$ mA/V²).
- (b) Find g_m and r_o if $V_A = 100$ V.
- (c) Draw the complete small signal equivalent circuit for the amplifier.
- (d) Find R_{in} , v_{gs}/v_{sig} , v_o/v_{gs} and v_o/v_{sig} and R_{out} .

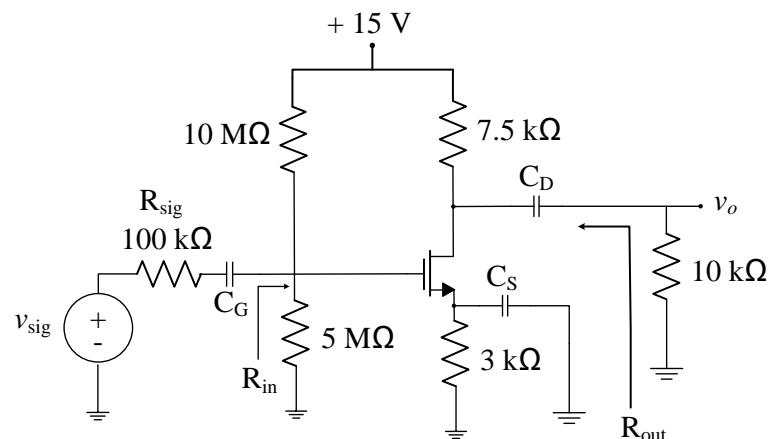**Fig. 2**


3. The NMOS transistor shown in **Fig. 3**, has $V_t = 0.9$ V and $V_A = 50$ V and operates with $V_D = 2$ V. What is the **voltage gain** v_o/v_i ? What do ‘ V_D ’ and “gain” become when ‘I’ is increased to 1 mA?

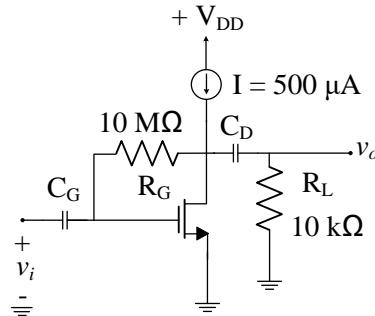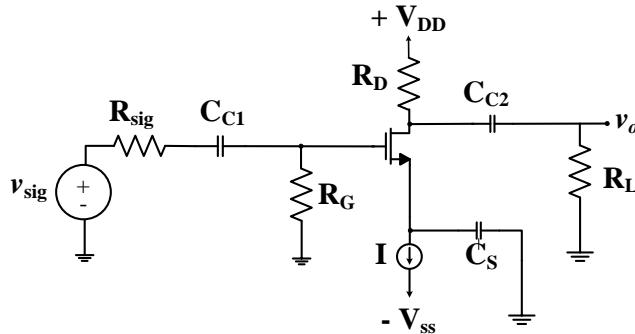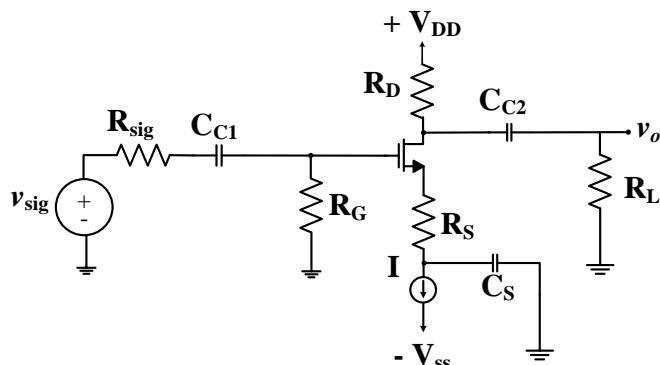**Fig. 3**


4. Calculate the overall voltage gain G_v (v_o / v_{sig}) of a common source amplifier, shown in **Fig. 4**, which has $g_m = 2 \text{ mA/V}$, $r_o = 50 \text{ k}\Omega$, $R_D = 10 \text{ k}\Omega$ and $R_G = 10 \text{ M}\Omega$. The amplifier is fed from a signal source with a resistance, R_{sig} of $0.5 \text{ k}\Omega$ and amplifier output is coupled to a load resistance, R_L of $20 \text{ k}\Omega$.

**Fig. 4**

5. The overall voltage gain of the amplifier shown in **Fig. 5** was measured with resistance R_s of $1\text{k}\Omega$ in place and found to be **-10**. When R_s is shorted, but the circuit operation remained linear the gain doubled. What must g_m be? What value of R_s is needed to obtain an overall voltage gain of **-8**?

**Fig. 5**

SOLN.① P-1

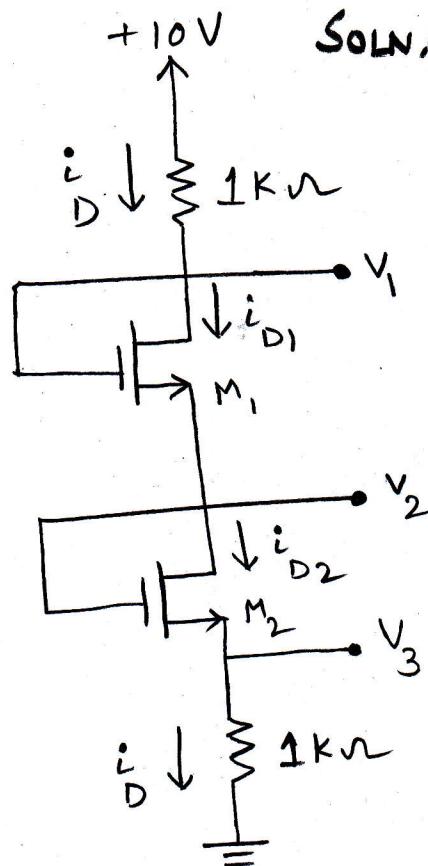

$$V_t = 1V$$

$$\frac{k'n}{L} \frac{W}{L} = 2 \text{ mA/V}^2$$

(=K, say)

if we consider both the devices M_1 & M_2 to be

identical, then

$$i_{D1} = i_{D2} = i_D \quad \text{where} \quad i_{D1} = \frac{1}{2} K (V_{GS1} - V_t)^2$$

$$i_{D2} = \frac{1}{2} K (V_{GS2} - V_t)^2$$

$$\Rightarrow V_{GS1} = V_{GS2}$$

$$\Rightarrow V_1 - V_2 = V_2 - V_3$$

$$\Rightarrow V_3 = 2V_2 - V_1 \quad \text{--- (2)}$$

$$\text{But, } i_D = \frac{V_3}{1000} = \frac{10 - V_1}{1000} \Rightarrow V_3 = 10 - V_1 \quad \text{--- (3)}$$

$$\text{from (2) \& (3), } 10 - V_1 = 2V_2 - V_1 \Rightarrow 2V_2 = 10$$

$$\Rightarrow \boxed{V_2 = 5V}$$

$$\text{from (1), take } \frac{i_{D2}}{i_D} = \frac{i_D}{i_D}$$

$$\Rightarrow \frac{1}{2} K (V_{GS2} - V_t)^2 = \frac{V_3}{1000}$$

$$\Rightarrow \frac{1}{2} \times 2 \times 10^{-3} \times (V_2 - V_3 - 1)^2 = \frac{V_3}{1000} \quad P-2$$

$$\Rightarrow V_3 = (V_2 - V_3 - 1)^2$$

$$\Rightarrow V_3 = (15 - V_3 - 1)^2 = (4 - V_3)^2$$

$$\Rightarrow V_3 = V_3^2 - 8V_3 + 16$$

$$\Rightarrow V_3^2 - 9V_3 + 16 = 0$$

on solving $V_3 = 6.56 \text{ V} ; 2.44 \text{ V}$

i) when $V_3 = 6.56 \text{ V}$

from ③,

$$V_1 = 10 - V_3 = 10 - 6.56 \\ = 3.44 \text{ V}$$

but

$$V_{GSI} = V_1 - V_2 = 3.44 - 5 \\ = -1.56 \text{ V}$$

this is not feasible since V_{GSI}^1 must be at least V_t , by L_{DI} to blow.

ii) when $V_3 = 2.44 \text{ V}$

$$\Rightarrow V_1 = 10 - V_3 \quad (\because \text{from } ③)$$


$$= 10 - 2.44 = 7.56 \text{ V}$$

which is sufficient to make $V_{GSI} \geq V_t$.

$$\therefore V_1 = 7.56 \text{ V} ; V_2 = 5 \text{ V} ; V_3 = 2.44 \text{ V}$$

SOLN. ②

P-3

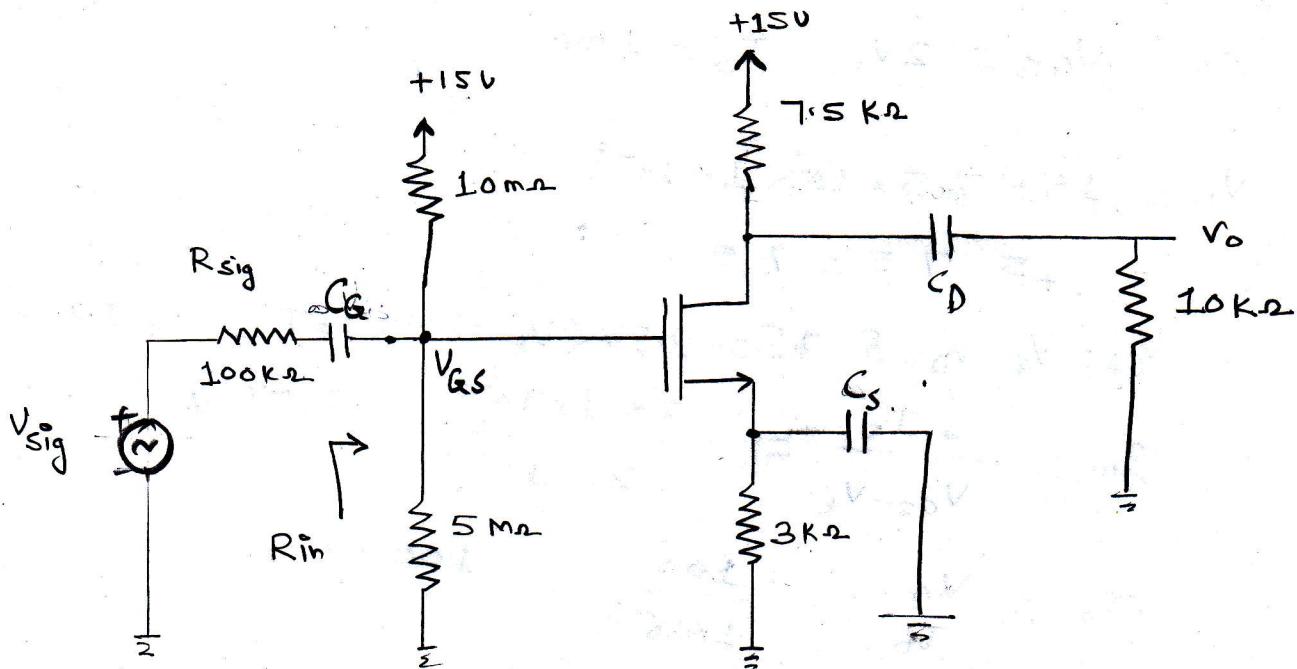

a) Given that $V_t = 1 \text{ V}$, $k_n \frac{\omega}{L} = 2 \text{ mA/V}^2$.

$$\therefore V_G = \frac{15 \times 5 \times 10^6}{10 \times 10^6 + 5 \times 10^6} = \frac{15 \times 5}{15} = 5 \text{ V.}$$

$$V_{DD} = 15 \text{ V}, \quad V_{GS} = V_G - V_S$$

$$\because V_S = 3I_D \quad \Rightarrow V_{GS} = 5 - 3I_D$$

$$\therefore I_D = \frac{k_n}{2} \times \frac{\omega}{L} (V_{GS} - V_t)^2 = \frac{2}{2} \times (5 - 3I_D - 1)^2$$

$$\Rightarrow I_D = (4 - 3I_D)^2 = 16 + 9I_D^2 - 24I_D$$

$$\Rightarrow 9I_D^2 - 25I_D + 16 = 0$$

$$\Rightarrow I_D = 1 \text{ mA} \quad \text{or} \quad I_D = 1.77 \text{ mA}$$

$$V_{GS} = 5 - 3I_D$$

$$\therefore V_{GS} = 5 - 3 \times 1$$

$$V_{GS} = 2 \text{ V}$$

$$\therefore V_{GS} = 5 - 3 \times 1.77$$

$$\therefore V_{GS} = -0.31 \text{ V} < V_t$$

$$so \quad V_{GS} = 2V, \quad I_D = 1mA$$

$$\Rightarrow V_D = 15 - 7.5 \times 10^3 \times 1 \times 10^{-3}$$

$$= 15 - 7.5 = 7.5V$$


$V_{GD} = V_G - V_D = 5 - 7.5 = -2.5V < V_t \Rightarrow$ MOSFET is in saturation.

$$b) \quad g_m = \frac{2 I_D}{V_{GS} - V_t} = \frac{2 \times 1 \times 10^{-3}}{2 - 1} = 2 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{100}{1 \times 10^{-3}} = 100 \text{ k}\Omega$$

$$(g_m = \frac{2I_D}{2V_{GS}} = \frac{2}{2V_{GS}} \left[\frac{1}{2} K_n' \frac{W}{L} (V_{GS} - V_t)^2 \right] = K_n' \frac{W}{L} (V_{GS} - V_t) = \frac{2I_D}{V_{GS} - V_t})$$

∴

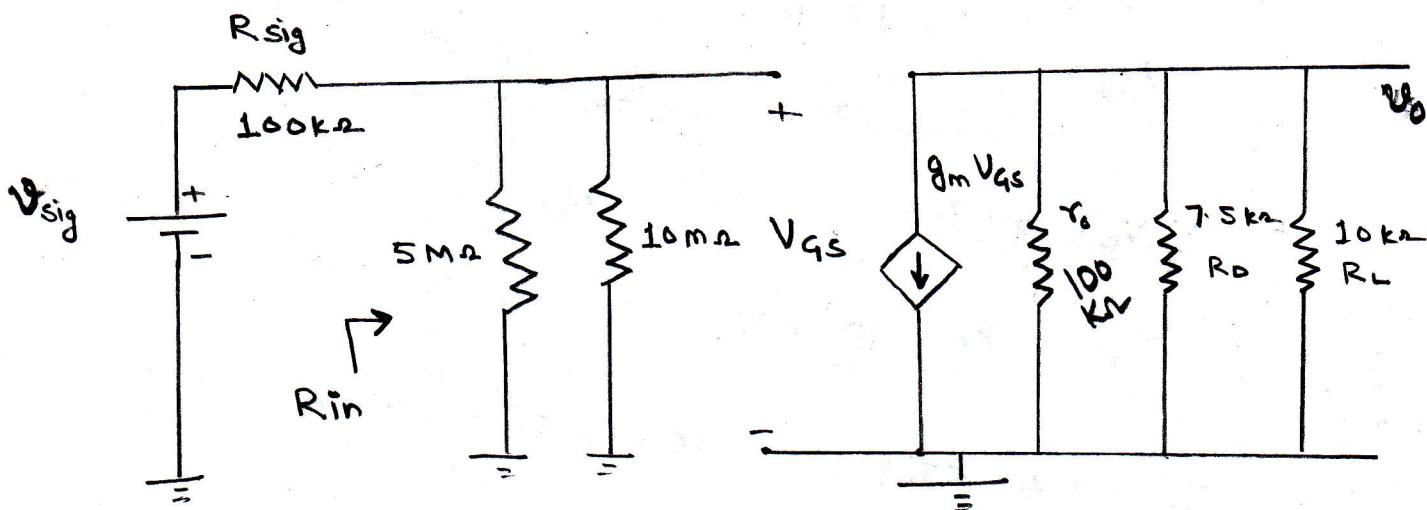

$$d) \quad R_{in} = 5M\Omega \parallel 10M\Omega = \frac{5M \times 10M}{5M + 10M} = 3.33M\Omega$$

$$V_{GS} = V_{sig} \times \frac{R_{in}}{R_{in} + R_{sig}} \Rightarrow \frac{V_{GS}}{V_{sig}} = \frac{3.33 \times 10^6}{100 \times 10^3 + 3.33 \times 10^6}$$

$$\Rightarrow \frac{v_{gs}}{v_{sig}} = \frac{3.33}{0.1 + 3.33} = 0.97$$

$$\Rightarrow \therefore v_o = -g_m v_{gs} (r_o \parallel R_D \parallel R_L)$$


$$\Rightarrow \frac{v_o}{v_{gs}} = -2 \times 10^{-3} \times 4.1 \times 10^3 = -8.2$$

$$\Rightarrow \frac{v_o}{v_{sig}} = \frac{v_o}{v_{gs}} \times \frac{v_{gs}}{v_{sig}} = -8.2 \times 0.97 = -7.95$$

$$\begin{aligned} R_{out} &= r_o \parallel R_D \parallel R_L \\ &= 100\text{k}\Omega \parallel 7.5\text{k}\Omega \parallel 10\text{k}\Omega \\ &= 4.1 \text{ k}\Omega \end{aligned}$$

SOLN ③

P-6

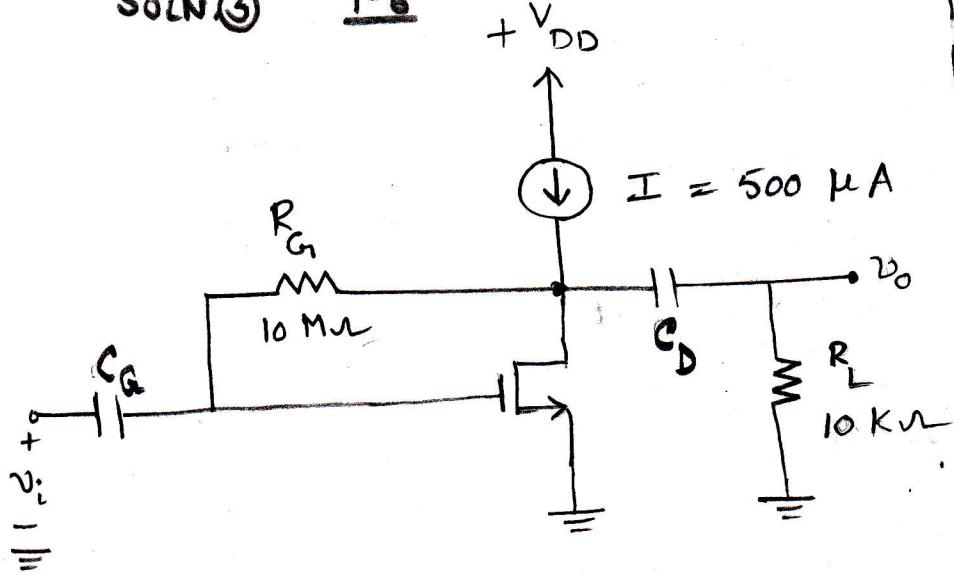


For MOSFET to operate in saturation,
 $V_{GS} > V_t$ - (i)
and $V_{DS} > (V_{GS} - V_t)$ - (ii)
 $\Rightarrow V_t > V_{GS} - V_{DS}$
 $V_t > V_{GD}$

For this ckt $V_{GD} \neq 0$
as no current flow in R_G for DC analysis,
 $V_t = 0.9 \text{ V} > (V_{GD} = 0)$
 $(V_{GS} = V_{DS} = V_D = 2 \text{ V}) > V_t$

given $V_t = 0.9 \text{ V}$; $V_A = 50 \text{ V}$ with $V_D = 2 \text{ V}$

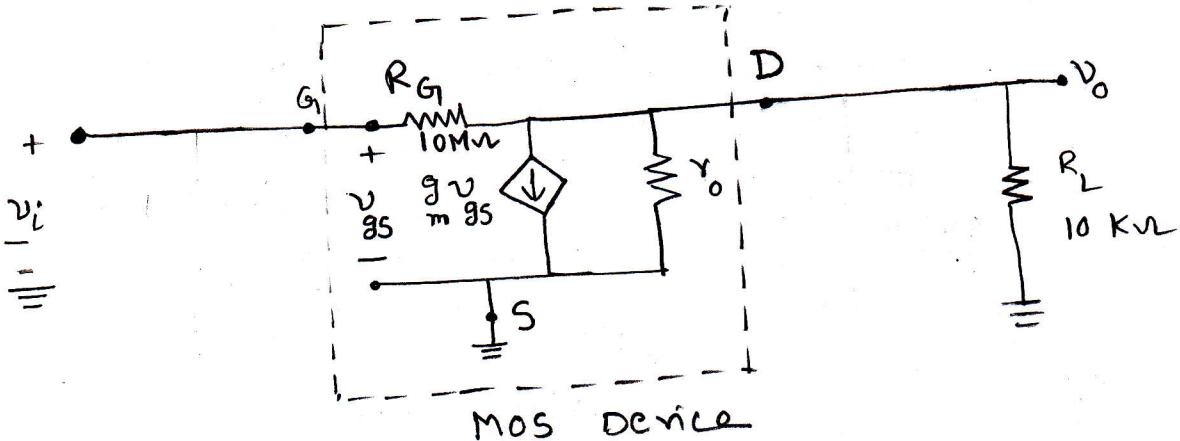The ac equivalent circuit of the Amplifier is,



The Dotted box has,

$$r_o = \frac{V_A}{I_D} = \frac{50}{0.5 \times 10^{-3}}$$

$$\therefore \frac{I_D}{r_o} = I = 0.5 \text{ mA}$$

↓ DC current

$$= 100 \text{ k}\Omega$$

$$g_m = \frac{2 I_D}{V_{GS} - V_t} = \frac{2 \times 0.5 \times 10^{-3}}{2 - 0.9}$$

$$= \frac{10^{-3}}{1.1} = 0.91 \text{ mA/V}$$

Since R_G is large
 $V_{GS} = V_{DS} = V_D$

$$\left[I_D = \frac{k}{2} (V_{GS} - V_t)^2 \Rightarrow g_m = \frac{\partial I_D}{\partial V_{GS}} = K (V_{GS} - V_t) \Rightarrow g_m = \frac{2 I_D}{V_{GS} - V_t} \right]$$

from the figure,

P-7

$$\begin{aligned} v_o &\approx -g_m v_{gs} [v_o \parallel R_L] \text{ as } R_G \gg r_{o1} \parallel R_D \parallel R_L \\ &= -g_m v_i [v_o \parallel R_L] \\ \Rightarrow \frac{v_o}{v_i} &= -g_m [v_o \parallel R_L] \\ &= -0.91 \times 10^{-3} [100K \parallel 10K] \\ &= -0.91 \times 10^{-3} \times \left[\frac{100 \times 10}{100 + 10} \right] \times 10^3 \end{aligned}$$

$$\Rightarrow A_v = \frac{v_o}{v_i} = -8.27$$

$$\therefore \boxed{\text{ac voltage gain} = \frac{v_o}{v_i} = -8.27}$$

When $I = 1\text{mA}$, (that is ' I is doubled)

then,

$$\frac{I_{D,\text{new}}}{I_{D,\text{old}}} = \frac{[V_{GS,\text{new}} - V_t]^2}{[V_{GS,\text{old}} - V_t]^2} = 2$$

$$\Rightarrow V_{GS,\text{new}} = V_t + \sqrt{2} [V_{GS,\text{old}} - V_t]$$

$$= 0.9 + \sqrt{2} (2 - 0.9)$$

$$= 0.9 + 1.56 = 2.46 \text{ V} = V_{D,\text{new}}$$

which implies,

$$\frac{g_{m,\text{new}}}{g_{m,\text{old}}} = \sqrt{\frac{I_{D,\text{new}}}{I_{D,\text{old}}}} = \sqrt{2} \quad \begin{cases} I_D = \frac{1}{2} k (V_{GS} - V_t)^2 \\ g_m = \frac{\partial I_D}{\partial V_{GS}} = k (V_{GS} - V_t) \\ \therefore g_m \propto \sqrt{I_D} \end{cases}$$

$$\Rightarrow g_{m,\text{new}} = \sqrt{2} \times 0.91 \text{ mA/V} = 1.3 \text{ mA/V}$$

Also,

$$\frac{r_{o,new}}{r_{o,old}} = \frac{I_{D,old}}{I_{D,new}} = \frac{1}{2}$$

$$\Rightarrow r_{o,new} = \frac{r_{o,old}}{2} = \frac{100\text{ k}}{2} = 50\text{ k}\Omega$$

Then,


$$A_{v,new} = -g_{m,new} \left[r_{o,new} || R_L \right]$$

$$= -1.3 \times 10^{-3} \times \frac{50\text{k} \times 10\text{k}}{50\text{k} + 10\text{k}}$$

$$= -1.3 \times \frac{500}{60} = -10.833 \text{ V/V}$$

$$V_{D,new} = 2.46\text{ V}$$

$$A_{v,new} = -10.833 \text{ V/V}$$

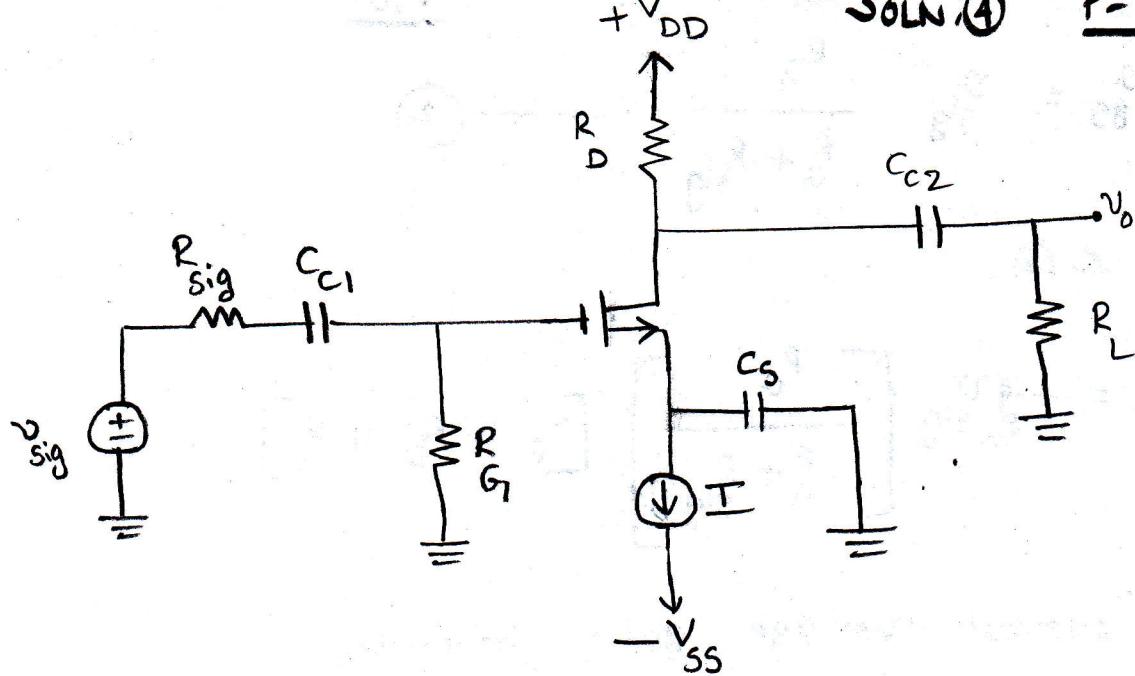

given

$$g_m = 2 \text{ mA/V}$$

$$R_D = 10 \text{ k}\Omega$$


$$\gamma_0 = 50 \text{ k}\Omega$$

$$R_{G1} = 10 \text{ M}\Omega$$

$$R_{\text{sig}} = 0.5 \text{ M}\Omega$$

$$R_L = 20 \text{ k}\Omega$$

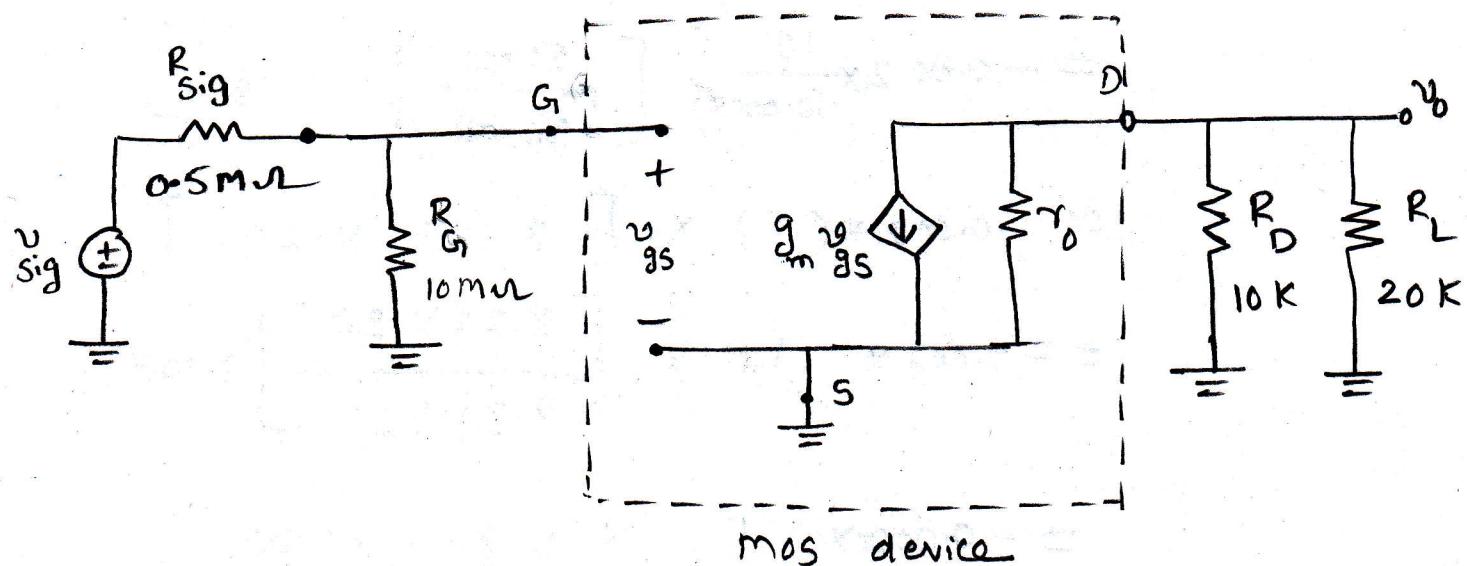The equivalent circuit of the CS Amplifier is,



from the figure,

$$v_o = -g_m v_{gs} [\gamma_0 \parallel R_D \parallel R_L] \quad \text{--- ①}$$

$$\frac{v_o}{v_{sig}} = \frac{R_G}{R_G + R_{sig}} \quad \text{--- (2)}$$

From ① & ②,

$$v_o = -g_m v_{sig} \left[\frac{R_G}{R_G + R_{sig}} \right] \quad [r_o \parallel R_D \parallel R_L]$$

The overall voltage gain becomes,

$$G_v = \frac{v_o}{v_{sig}} = - \frac{g_m R_G}{R_G + R_{sig}} \quad [r_o \parallel R_D \parallel R_L]$$

$$\Rightarrow G_v = -2 \times 10^{-3} \times \frac{10M}{10M + 0.5K} \quad [50K \parallel 10K \parallel 20K]$$

$$= -0.002 \times \frac{10}{10.0005} \left\{ \left[\frac{50 \times 10}{50+10} \right] K \parallel 20K \right\}$$


$$\approx -0.002 \times (1) \times [8.33K \parallel 20K]$$

$$= -0.002 \times \frac{8.33 \times 20}{8.33 + 20} \times 1000$$


$$= -0.002 \times 1 \times 5.882 \times 1000$$

$$= -11.76$$

$$\therefore G_v = -11.76 \text{ V/V}$$

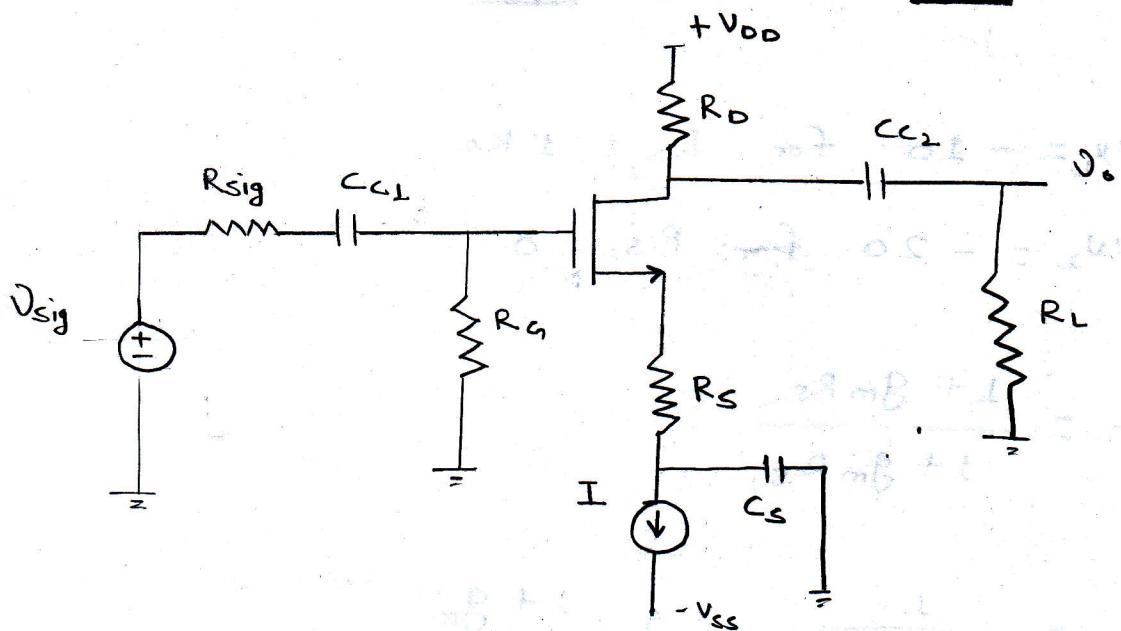

Equivalent circuit of Amplifier is.

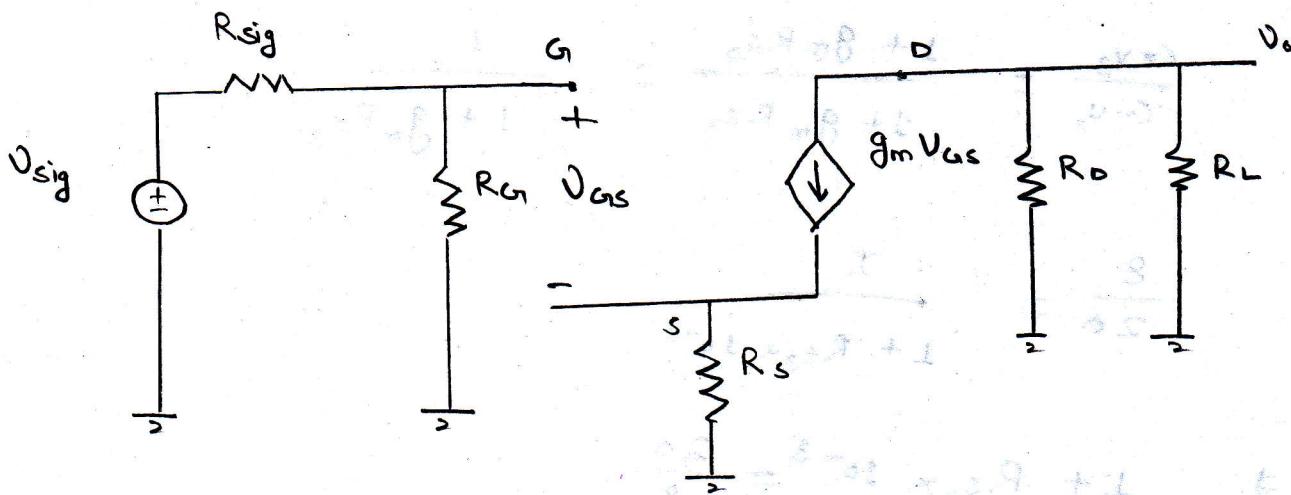

$$\therefore G_V = - \frac{R_G}{R_G + R_{sig}} \times \frac{\text{g}_m (R_D \parallel R_L)}{1 + \text{g}_m R_S}$$


Small-signal Equivalent Circuit: Neglecting r_o

$$v_{in} = v_{gs} + g_m v_{gs} R_s$$

$$v_o = -g_m v_{gs} (R_D \parallel R_L)$$

Voltage gain
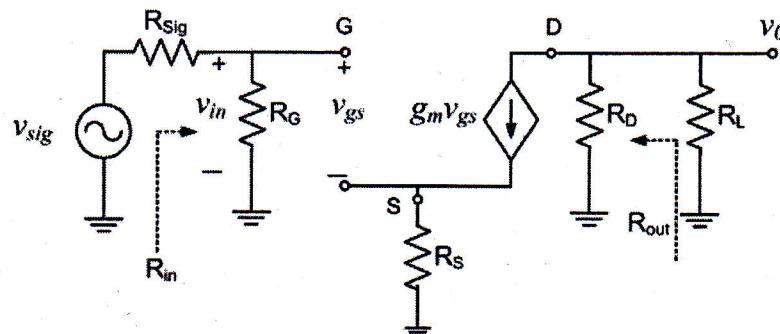
$$A_v = \frac{v_o}{v_{in}} = -\frac{g_m (R_D \parallel R_L)}{1 + g_m R_s}$$




52

Overall voltage gain

$$v_{in} = \frac{R_G}{R_G + R_{sig}} v_{sig}$$
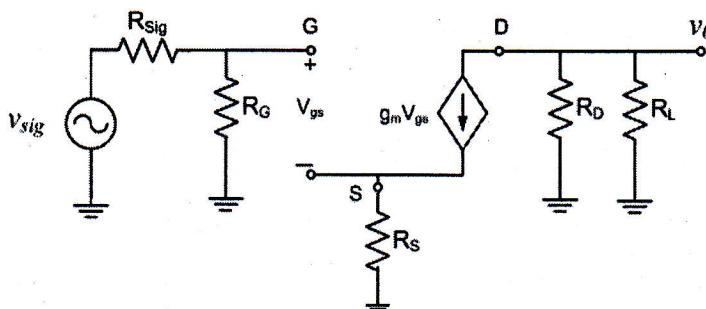
$$G_v = \frac{v_o}{v_{sig}} = -\frac{R_G}{R_G + R_{sig}} \frac{g_m (R_D \parallel R_L)}{1 + g_m R_s}$$



53

$$Gv_1 = -10 \text{ for } RS_1 = 1 \text{ k}\Omega$$

$$Gv_2 = -20 \text{ for } RS_2 = 0.$$

$$\frac{Gv_1}{Gv_2} = \frac{L + g_m RS_2}{L + g_m RS_1}$$

$$\Rightarrow \frac{10}{20} = \frac{L}{L + g_m \times 10^3} \Rightarrow L + g_m \times 10^3 = 2$$

$$\Rightarrow g_m = 1 \text{ mA/V.}$$

$$\Rightarrow \therefore Gv_3 = -8.$$

$$\Rightarrow \frac{Gv_3}{Gv_2} = \frac{L + g_m RS_3}{L + g_m RS_2} = \frac{L}{L + g_m RS_3}$$

$$\Rightarrow \frac{8}{20} = \frac{L}{L + RS_3 \times 10^{-3}}$$

$$\Rightarrow L + RS_3 \times 10^{-3} = \frac{20}{8}$$

$$\Rightarrow RS_3 = 1.5 \text{ k}\Omega$$

$\therefore RS_3 = 1.5 \text{ k}\Omega$ for voltage gain of -8.