

3rd August, 2016**Home Assignment 1**

1. In the circuit given in **Fig. 1** use nodal analysis to find the value of ' k ' that will cause ' V_y ' to be zero.

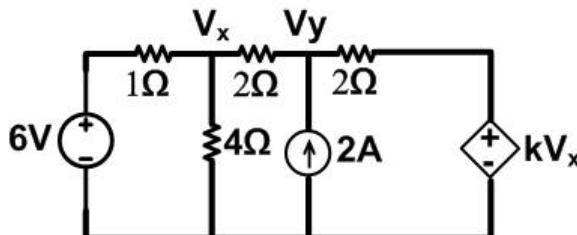


Fig. 1

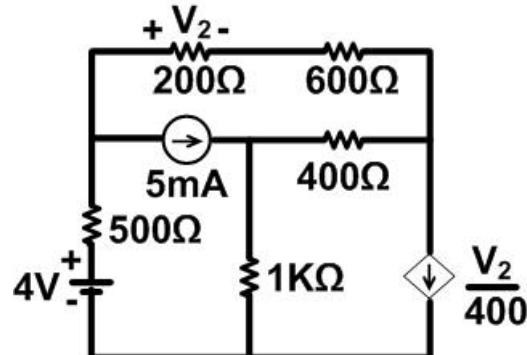


Fig. 2

2. Use mesh analysis on the circuit shown in **Fig. 2** to find the power supplied by the 4V battery.
 3. Use super mesh analysis to determine the voltage drop 'V' across **5Ω** resistor as shown in **Fig. 3**.

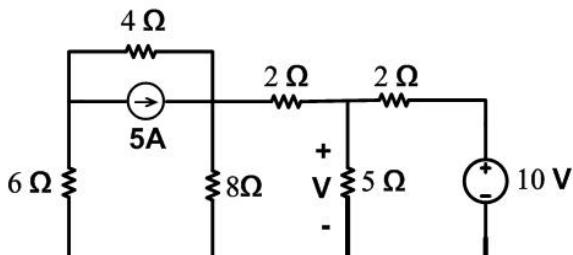


Fig. 3

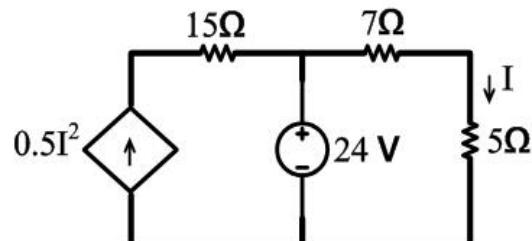


Fig. 4

4. In **Fig. 4**, determine the power delivered by the dependent source.
 5. In the circuit of the **Fig. 5**, determine the maximum positive current to which the source ' I_x ' can be set before any resistor exceeds its power rating.

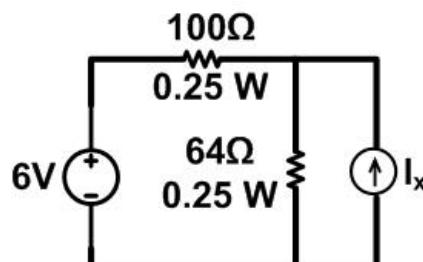


Fig. 5

6. Use the superposition theorem to find 'i' in **Fig. 6**.
7. For the circuit shown in **Fig. 7**, find 'R' so that power supplied by both the sources is equal to each other.

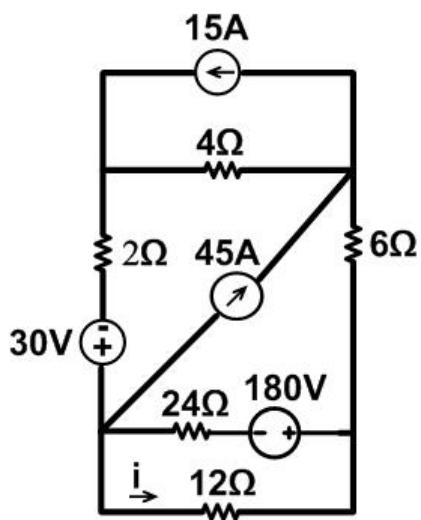


Fig. 6


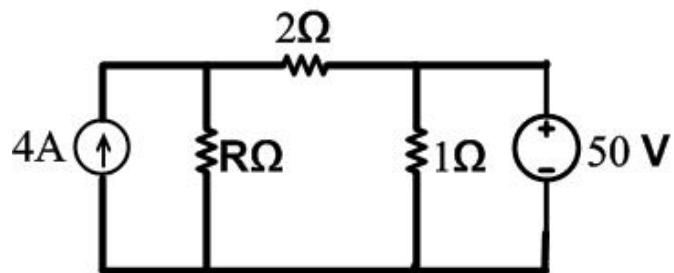


Fig. 7

SOLN. ①.

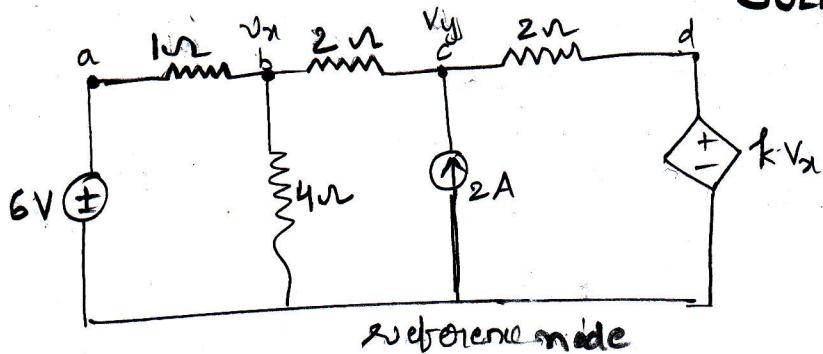

At nodes 'a' and 'd', we have

$$v_a = 6V ; v_d = k v_x$$

At nodes 'b' and 'c', we can write that

$$\frac{v_x - 6}{1} + \frac{v_x - v_y}{2} + \frac{v_x}{4} = 0 \quad \text{--- (1)}$$

$$\frac{v_y - v_x}{2} + \frac{v_y - kv_x}{2} = 2 \quad \text{--- (2)}$$

Put $v_y = 0$ for binding \star

From ①,

$$\frac{v_x - 6}{1} + \frac{v_x}{2} + \frac{v_x}{4} = 0$$

$$\Rightarrow 6 = v_x \left(\frac{7}{4} \right)$$

$$\Rightarrow v_x = \frac{24}{7} V$$

From ②,


$$\frac{v_x}{2} + \frac{kv_x}{2} = -2$$

$$\Rightarrow (1+k) \frac{v_x}{2} = -2$$

$$\Rightarrow 1+k = -\frac{4}{v_x} = -\frac{4}{(24/7)} = -\frac{28}{24}$$

$$\Rightarrow k = -1 - \frac{28}{24} = -\frac{52}{24} = -\frac{13}{6}$$

$\therefore k = -\frac{13}{6}$

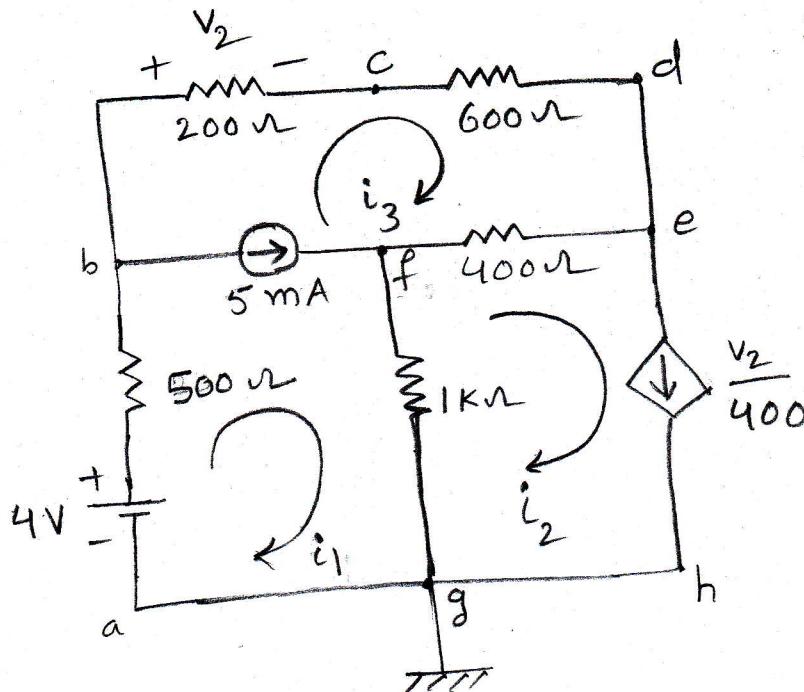

$$\text{in branch 'bf'} \rightarrow i_1 - i_3 = \frac{5}{1000}$$

$$\Rightarrow 1000i_1 - 1000i_3 = 5 \quad \textcircled{1}$$

for loop "abcdefga":

$$-4 + 500i_1 + 200i_3 + 600i_3 + 400(i_3 - i_2) + 1000(i_1 - i_2) =$$

$$\Rightarrow -4 + 1500i_1 - 1400i_2 + 1200i_3 = 0 \quad \textcircled{2}$$

$$\text{and from the figure, } V_2 = 200i_3 \quad \textcircled{3}$$

$$\text{in branch 'eh'} \rightarrow i_2 = \frac{V_2}{400} = \frac{200i_3}{400} \quad [\because \text{from } \textcircled{3}]$$

$$\Rightarrow i_2 = \frac{i_3}{2} \quad \textcircled{4}$$

from $\textcircled{2}$ & $\textcircled{4}$,

$$-4 + 1500i_1 - 1400\left(\frac{i_3}{2}\right) + 1200i_3 = 0$$


$$\Rightarrow 1500i_1 + 500i_3 = 4 \quad \textcircled{5}$$

$$\textcircled{1} \times 1 \Rightarrow 1000i_1 - 1000i_3 = 5$$

$$\textcircled{5} \times 2 \Rightarrow 3000i_1 + 1000i_3 = 8$$

$$\frac{4000i_1 = 13}{4000i_1 = 13} \Rightarrow i_1 = \frac{13}{4000} \text{ Amp}$$
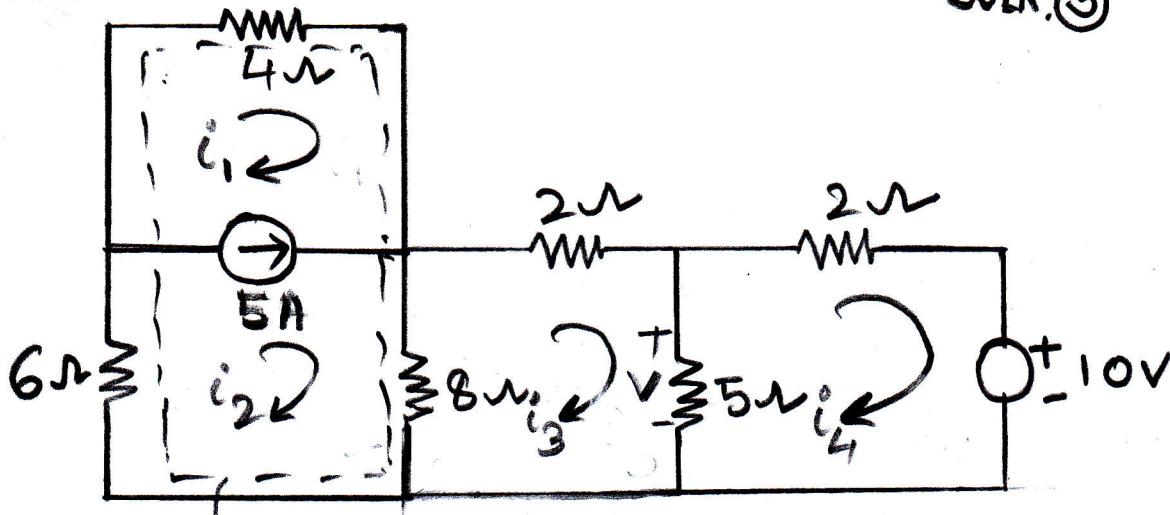
$$\therefore \text{Power generated by } 4V \text{ battery is, } P_{\text{gen}} = 4 \times \frac{13}{4000} W \\ = 13 \text{ mW.}$$



→ Supermesh

Applying KVL to the Supermesh.

$$4i_1 + 8(i_2 - i_3) + 6i_2 = 0 \quad \dots \dots \dots \textcircled{1}$$

$$i_2 - i_1 = 5. \quad \dots \dots \dots \textcircled{2}$$

Applying KVL to Mesh 3,

$$2i_3 + 5(i_3 - i_4) + 8(i_3 - i_2) = 0 \quad \dots \dots \dots \textcircled{3}$$

Applying KVL to Mesh 4,

$$2i_4 + 10 + 5(i_4 - i_3) = 0 \quad \dots \dots \dots \textcircled{4}$$

Equations 1, 2, 3, 4 can be rearranged as,

$$4i_1 + 14i_2 - 8i_3 + 0 \cdot i_4 = 0$$

$$-i_1 + i_2 + 0 \cdot i_3 + 0 \cdot i_4 = 5$$

$$0i_1 - 8i_2 + 15i_3 - 5i_4 = 0$$

$$0i_1 + 0i_2 - 5i_3 + 7i_4 = -10$$

NOW, applying cramer's rule we can obtain,

P4

$$\begin{vmatrix} 4 & 14 & 0 & 0 \\ -1 & 1 & 5 & 0 \\ 0 & -8 & 0 & -5 \\ 0 & 0 & -10 & 7 \end{vmatrix}$$

$$i_3 = \frac{1}{\begin{vmatrix} 4 & 14 & -8 & 0 \\ -1 & 1 & 0 & 0 \\ 0 & -8 & 15 & -5 \\ 0 & 0 & -5 & 7 \end{vmatrix}}$$

$$= \frac{220}{992} \simeq 0.22 \text{ A}$$

$$i_4 = \frac{1}{\begin{vmatrix} 4 & 14 & -8 & 0 \\ -1 & 1 & 0 & 5 \\ 0 & -8 & 15 & 0 \\ 0 & 0 & -5 & -10 \end{vmatrix}}$$

$$\begin{vmatrix} 4 & 14 & -8 & 0 \\ -1 & 1 & 0 & 0 \\ 0 & -8 & 15 & -5 \\ 0 & 0 & -5 & 7 \end{vmatrix}$$

$$= -\frac{1260}{992} \simeq -1.27 \text{ A}$$


∴ Voltage drop across 5Ω

$$= 5(i_3 - i_4) = 7.45 \text{ Volt}$$

SOLN. ④.

P-5

$$I = \frac{24}{7+5} = 2 A$$

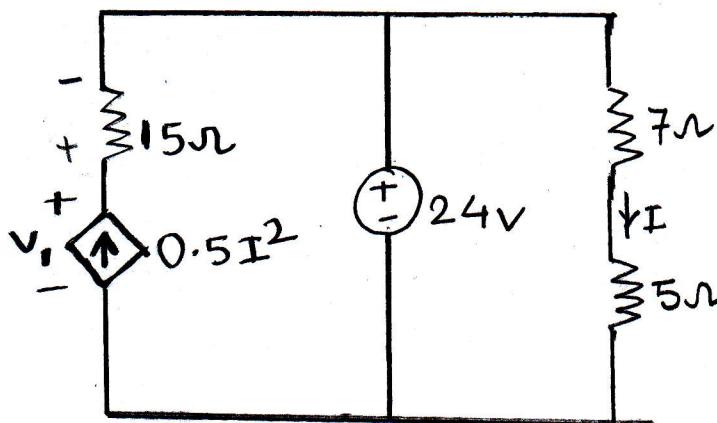

$$\begin{aligned}\therefore \text{Strength of the dependent current source} &= 0.5I^2 \\ &= 0.5 \times 2^2 \\ &= 0.5 \times 4 \\ &= 2 A\end{aligned}$$

$$24 - V_1 + 0.5I^2 \times 15 = 0$$

$$24 = V_1 - 0.5I^2 \times 15$$

$$\Rightarrow 24 = V_1 - 30$$

$$\Rightarrow V_1 = 54 V$$

Hence, Power delivered by the dependent source

$$= V_1 \times 0.5I^2$$


$$= 54 \times 2$$

$$= 108 W$$

(Note:- Current flows from - to + terminal of the dependent source \Rightarrow hence, it is delivering power).

SOLN. ⑤

P-6

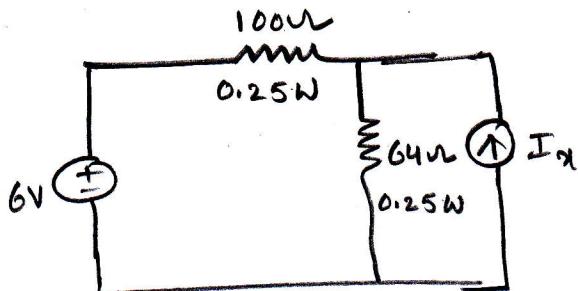

Each resistor is rated to a max. of 250mW.

If this value is exceeded by forcing too much current through resistors, excessive heating will occur leading to ckt damage.

Now 6V source cannot be changed

only I_x can be suitably chosen such that max current through resistors is not exceeded.


Based on 250mW power rating,

$$\text{max current through } 100\Omega = i_{100} = \sqrt{\frac{0.25}{100}} = 50\text{ mA} \quad \text{--- (1)}$$

Similarly current through 64Ω resistor = $i_{64} = 62.5\text{ mA}$

We use superposition principle because unlike Nodal and mesh analysis methods, superposition allows us to identify the effect of the current source I_x separately

Consider only 6V source in the given ckt

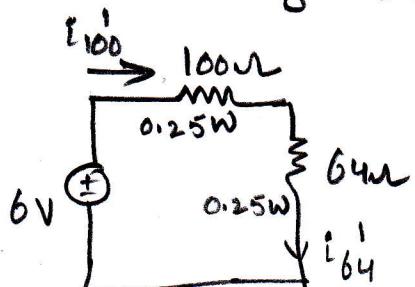


$$i_{100} = \frac{6}{164} = \frac{i_1}{64} = 36.59\text{ mA} \quad \text{--- (3)}$$

\Rightarrow 6V source acting alone does not pose any overheating problems for either resistor

For the circuit only with current source I_x present,

Using current division we have

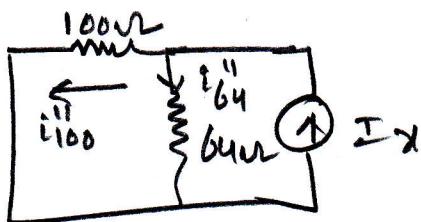

$$i_{100}'' = \frac{I_x \cdot 64}{164} \quad - (4)$$

$$i_{64}'' = \frac{100}{164} I_x \quad - (5)$$

We note i_{64}'' adds to i_{64}' and
 i_{100}'' is opposite in direction to i_{100}'

$$\therefore I_x \text{ can supply contribute } 0 \text{ to } 62.5 - 36.59 \quad - (6)$$

$$= 25.91 \text{ mA} = i_{64}'' \text{ (max)} \\ (\text{to } 64\Omega \text{ resistor})$$

$$\text{and } 50 - (-36.59) = 86.59 \text{ mA} (\text{to } 100\Omega \text{ resistor}) \quad - (7)$$

$$= i_{100}'' \text{ (max)}$$

$$(\because \text{Note } (-i_{100}') + i_{100}'' \leq 50 \Rightarrow i_{100}'' = 50 + i_{100}')$$

Using current division, the 100Ω resistor places the following constraint on I_x : [from (4) & (7)]

$$I_x < 86.59 \times 10^{-3} \left(\frac{164}{64} \right)$$


$$< 221.9 \text{ mA}$$

and 64Ω resistor requires that [from (5) & (6)]

$$I_x < 25.91 \times 10^{-3} \left(\frac{164}{100} \right)$$

$$< 42.49 \text{ mA}$$

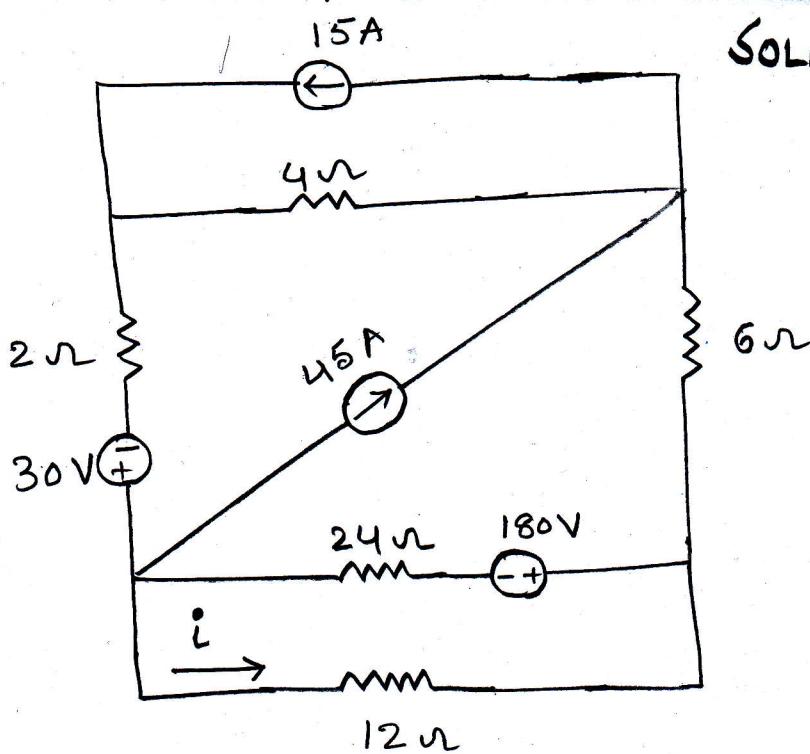
In order to meet both constraints, I_x must be less than 42.49 mA.



To apply the Superposition Principle,

- i) consider 15A source alone

Then the circuit reduces to

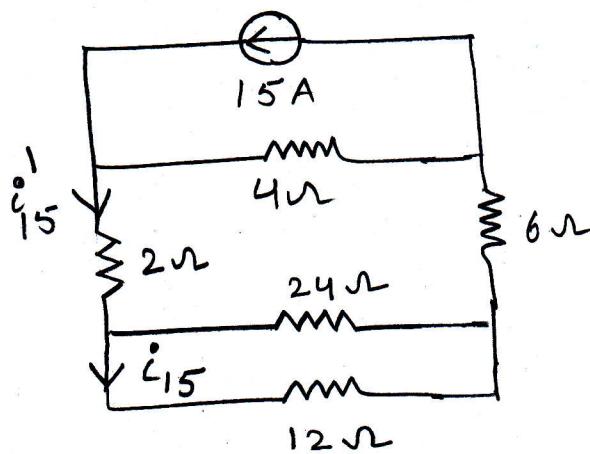

Using the current division rule we have,

$$\begin{aligned}
 i_{15} &= \frac{4}{4 + [2 + 6 + (24 \parallel 12)]} \times 15A \\
 &= \frac{4}{4 + 2 + 6 + 8} \times 15A \\
 &= \frac{4}{20} \times 15A = 3A
 \end{aligned}$$


Pg

Now,

$$\begin{aligned}
 i_{15} &= \frac{24}{24+12} \times i_1 \\
 &= \frac{24}{36} \times 3A \\
 &= 2A \\
 \therefore i_{15} &= 2A
 \end{aligned}$$

ii) consider 30V source alone

Then the circuit reduces to

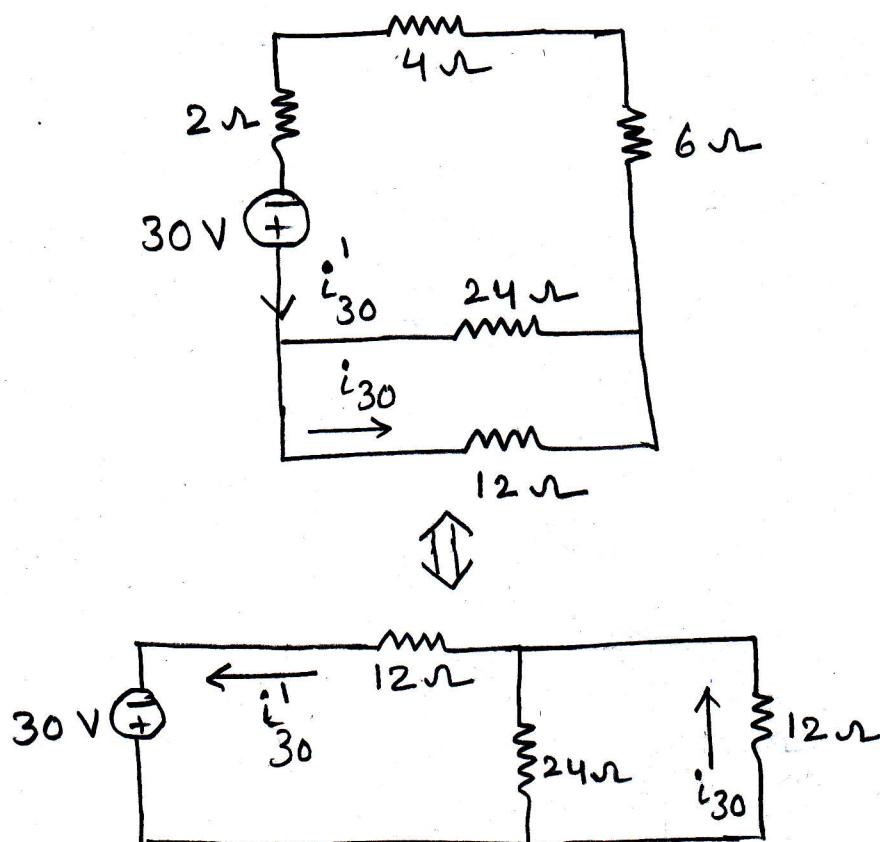

Now i_30^1 can be bound as,

$$\Rightarrow i_30^1 = \frac{30}{12 + [24 \parallel 12]}$$

$$= \frac{30}{12 + 8} = \frac{30}{20} = 1.5A$$


NOW Using the current division rule,

$$\begin{aligned} i_{30} &= \frac{24}{24+12} \times i_1 \\ &= \frac{24}{36} \times 1.5 \text{ A} \\ &= 1 \text{ A} \end{aligned}$$

$$\therefore i_{30} = 1 \text{ A}$$

iii) consider 180V source alone.

Then the circuit reduces to

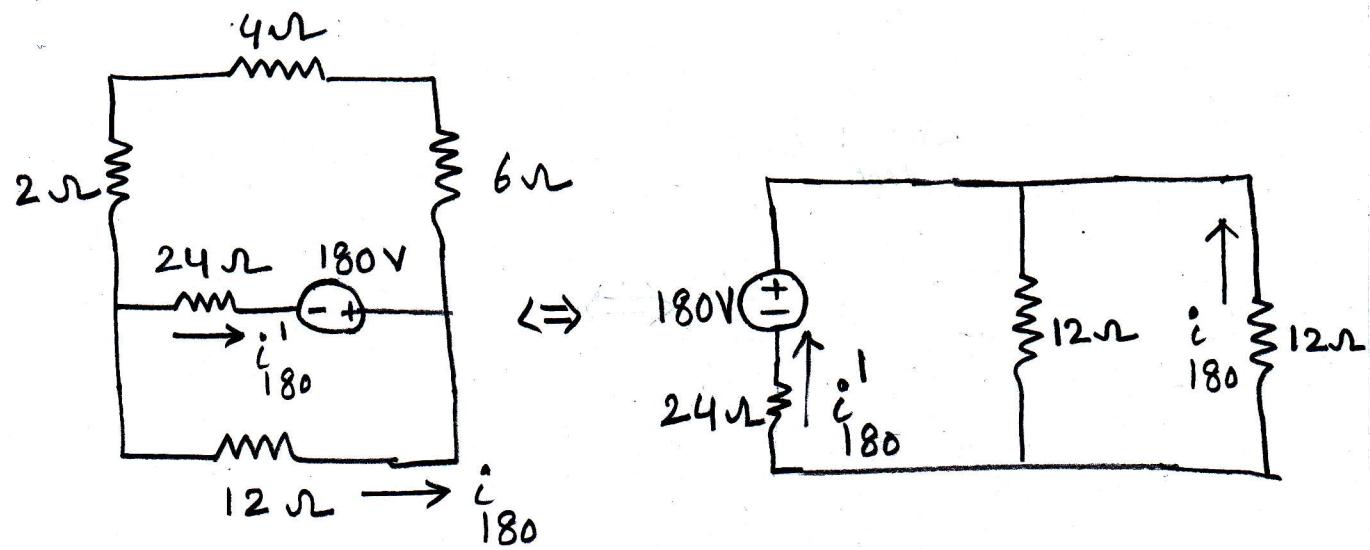

Now i_180^1 can be found as


$$\begin{aligned} \Rightarrow i_1^1 &= \frac{180}{24 + [12 \parallel 12]} \\ &= \frac{180}{24 + 6} = \frac{180}{30} = 6 \text{ A} \end{aligned}$$

Now from current division rule,

$$\begin{aligned}
 i_{180} &= -\frac{12}{12+12} \times i_{180}^1 \\
 &= -\frac{12}{24} \times 6A \\
 &= -3A
 \end{aligned}$$

$$i_{180} = -3A$$

iv) consider 45A source alone

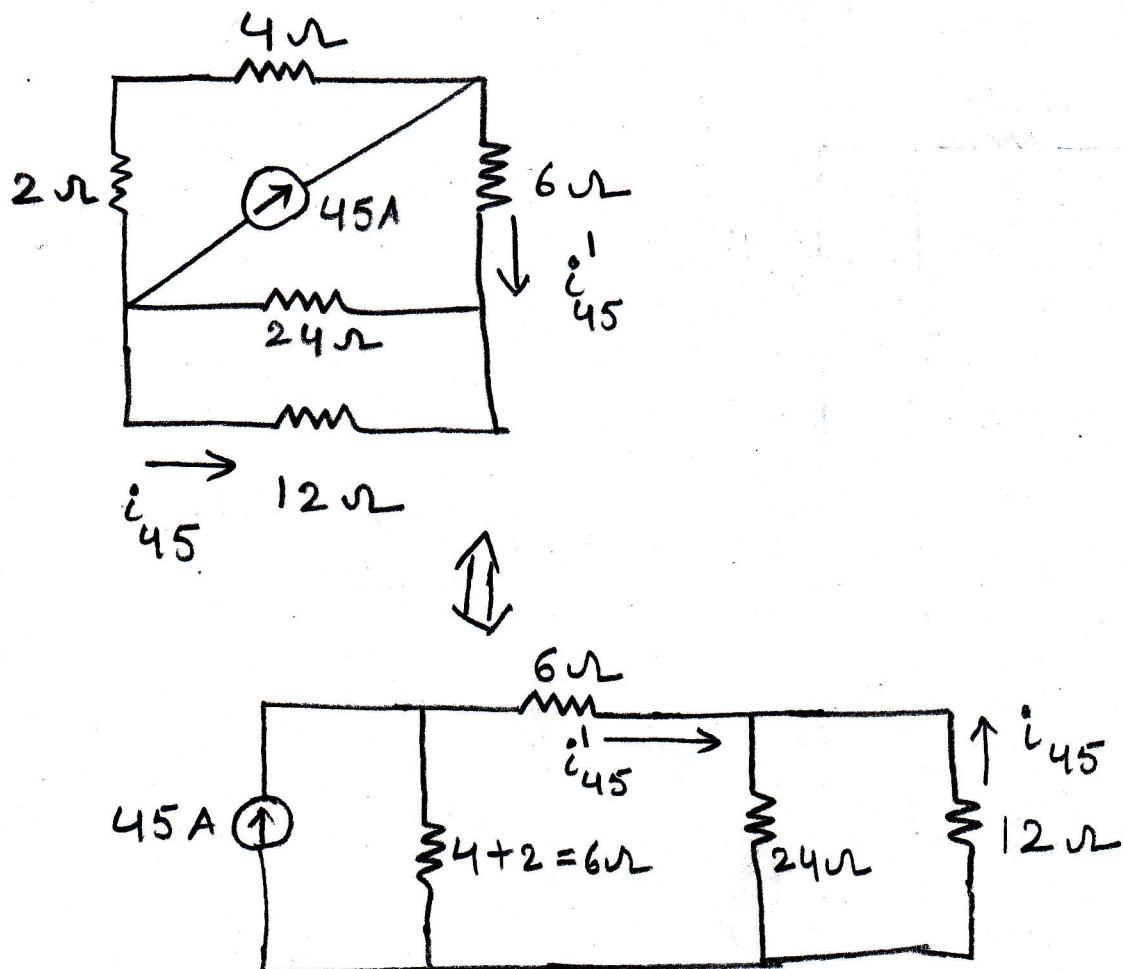

Now from the above circuit

$$i_{45}^1 = \frac{6}{6+6+[24 \parallel 12]} \times 45A$$

$$\Rightarrow i_{45}^o = \frac{6}{6+6+8} \times 45A \\ = 13.5A$$

NOW


$$i_{45} = - \frac{24}{24+12} \times i_{45}^o \\ = - \frac{24}{36} \times 13.5A \\ = -9A$$

$$i_{45} = -9A$$

NOW the desired current ' i ' can be written as,

$$i = i_{15} + i_{30} + i_{180} + i_{45} \\ = 2A + 1A - 3A - 9A \\ = -9A$$

$$\therefore i = -9A$$

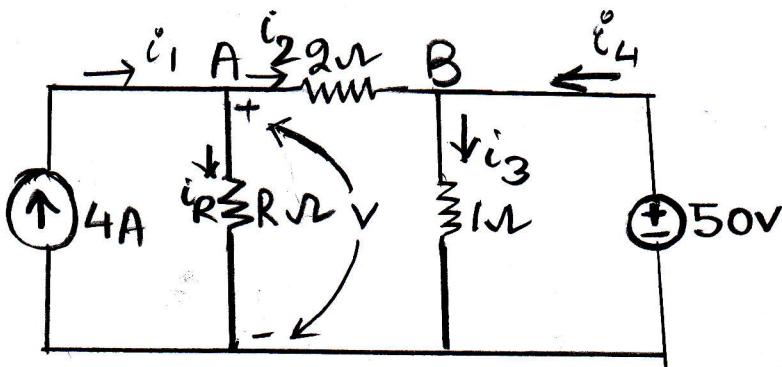

SOLN. ⑦

P-13

Node A :

$$-4 + \frac{v}{R} + \frac{v - 50}{2} = 0$$

Rearranging, $\frac{v}{R} + 0.5v = 29 \quad \dots \dots \text{(i)}$

At node B :

$$\frac{50-v}{2} + \frac{50}{1} - i_4 = 0$$

$$\Rightarrow -0.5v + 75 - i_4 = 0$$

$$\Rightarrow 0.5v + i_4 = 75 \quad \dots \dots \text{(ii)}$$

Solving (i) and (ii),

$$\frac{v}{R} - i_4 = -46$$

$$\Rightarrow i_4 = \frac{v}{R} + 46 \quad \dots \dots \text{(iii)}$$

since, power flow from both the sources are equal,

$$50i_4 = 4v \quad \dots \dots \text{(iv)}$$

From (iii) substituting the value of i_4 ,

$$50\left(\frac{v}{R} + 46\right) = 4v$$

$$\Rightarrow \frac{v}{R} + 46 = \frac{2v}{25} \quad \dots \dots \text{(v)}$$

From (ii) and (v),

$$\Rightarrow 29 - 0.5v + 46 = \frac{2v}{25}$$

$$\Rightarrow 75 = \frac{2V}{25} + 0.5V$$

$$\Rightarrow 75 = \frac{2 + 12.5}{25} \cdot V$$

$$= \frac{14.5}{25} V$$

$$\Rightarrow V = \frac{75 \times 25}{14.5}$$

$$= 129.3 \quad \text{--- --- (vi)}$$

Substituting the value of V in (i),

$$\frac{129.3}{R} + 0.5 + 129.3 = 29$$

$$\Rightarrow \frac{129.3}{R} + 64.65 = 29$$

$$\Rightarrow \frac{129.3}{R} = -35.65$$

$$\Rightarrow R = -\frac{129.3}{35.65} = -3.63 \Omega$$

Since the value of R comes out to be negative, so power supplied by both sources ^{not} can't be equal to each other for any practical (positive) value of R.