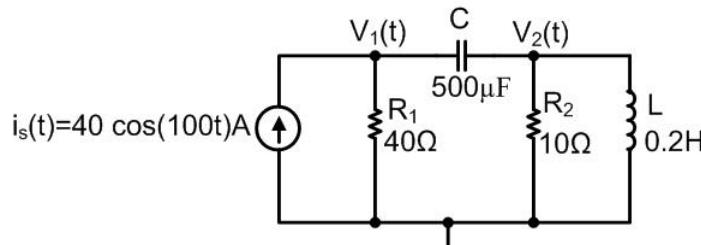
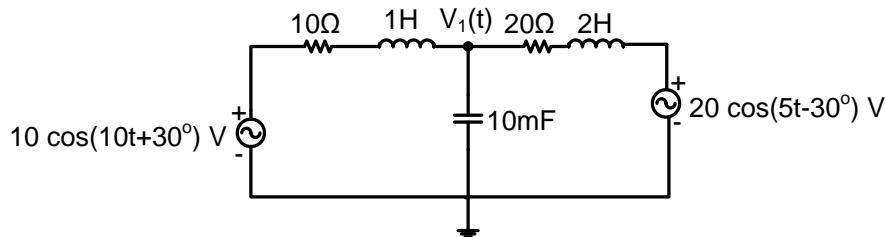


23<sup>rd</sup> August, 2016**Home Assignment – 4**

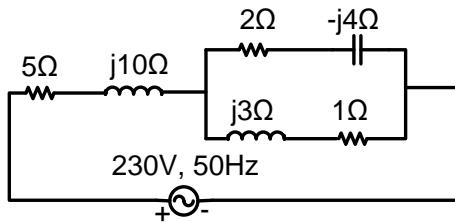
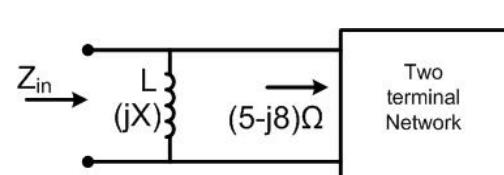
1. Using the node voltage method, determine the voltages  $V_1(t)$  and  $V_2(t)$  in the circuit shown in **Fig. 1**.

**Fig. 1**

2. Using the superposition theorem, find the voltage  $V_1(t)$  in the circuit shown in **Fig. 2**

**Fig. 2**

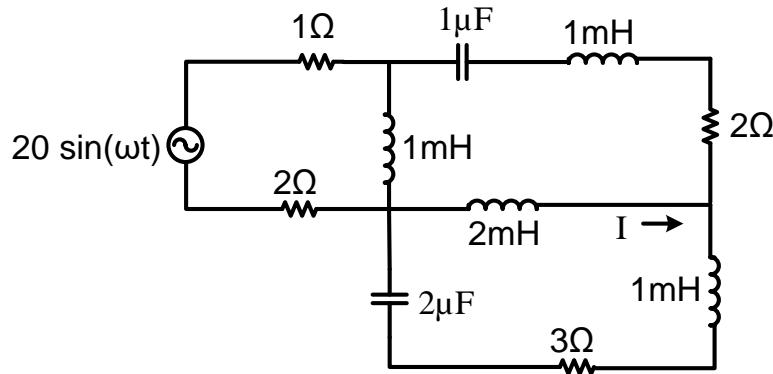
3. Find the **average power** and **reactive power**, in the network shown in **Fig. 3**.

**Fig. 3****Fig. 4**


4. The two terminals network shown in **Fig. 4**, has an input impedance of  $(5-j8) \Omega$ . At a frequency of 4 krad/s, what inductance should be placed in parallel with the network to cause the input impedance to:

- a) have zero reactance?
- b) have a magnitude of  $4 \Omega$ ?


5. Using the loop current method, find the current 'I' in the circuit shown in **Fig. 5**. Assume  $\omega = 10,000 \text{ rad/s}$ .

**Fig. 5**

6. For the circuit shown in **Fig. 6**,  $v_1 = 10\angle 0^\circ \text{ V}$  and  $i_1 = 10\angle 90^\circ \text{ mA}$  at  $\omega = 10^6 \text{ rad/s}$ . If the circuit is in steady state, find the current ' $i(t)$ ' through the inductor.

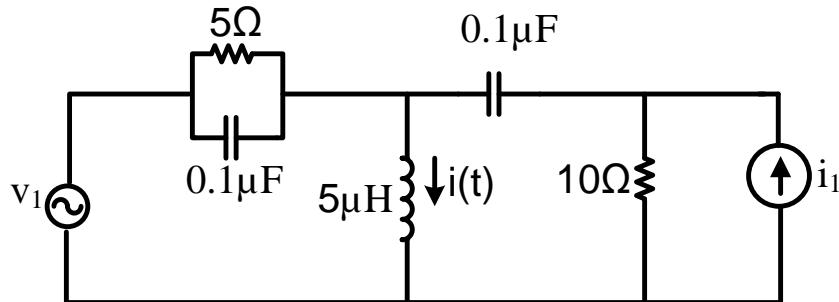**Fig. 6**

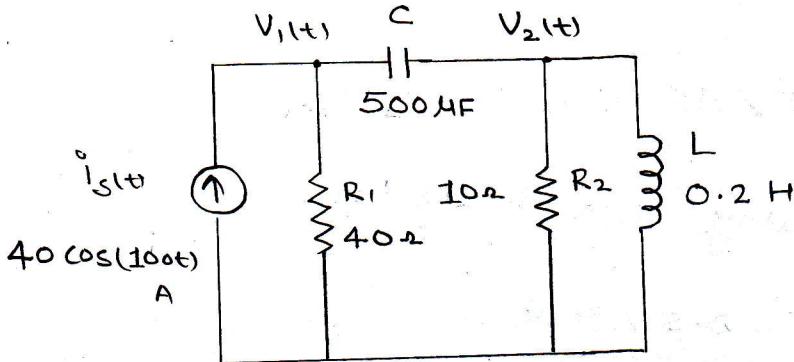7. In a series R-L-C circuit derive the expressions for frequency (a) at which the magnitude of voltage across the capacitor ( $V_c$ ) is maximum and (b) at which the magnitude of voltage across the inductor ( $V_L$ ) is maximum.




$$\omega = 100 \text{ rad/s.}$$

$$X_L = \omega L = 100 \times 0.2 = 20 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{10^6}{100 \times 500} = 20 \Omega$$

$$Z_L = jX_L; \quad Z_C = -jX_C$$

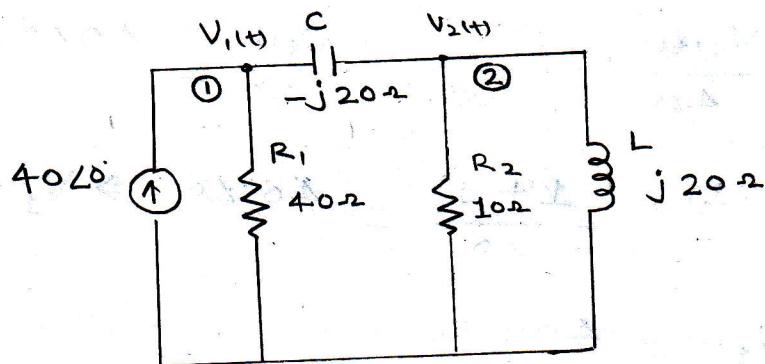

⇒ Applying node voltage method at node ① :-

$$-40 \angle 0^\circ + \frac{V_1(t)}{40} + \frac{V_1(t) - V_2(t)}{-j20} = 0 \quad -i)$$

⇒ Applying node voltage method at node ② :-

$$\frac{V_2(t)}{10} + \frac{V_2(t)}{j20} + \frac{V_2(t) - V_1(t)}{-j20} = 0$$

$$\Rightarrow \frac{V_2(t)}{10} + \frac{V_2(t)}{j20} = \frac{V_2(t) - V_1(t)}{j20} \quad -ii)$$

$$\Rightarrow \frac{V_2(t)}{10} + \frac{V_2(t)}{j20} = \frac{V_2(t)}{j20} - \frac{V_1(t)}{j20} \Rightarrow V_2(t) = j0.5 V_1(t)$$

$$\Rightarrow \frac{V_2(t)}{10} = -\frac{1}{j20} V_1(t)$$

$$\Rightarrow V_2(t) = 0.5 \angle 90^\circ V_1(t) \quad \text{--- iii)}$$

$\Rightarrow$  on substituting  $V_2(t)$  in eq. i)

$$\Rightarrow \frac{V_1(t)}{40} + \frac{V_1(t) - 0.5 \angle 90^\circ V_1(t)}{-j20} = 40 \angle 0^\circ$$

$$\Rightarrow \frac{V_1(t)}{40} + \frac{jV_1(t)}{20} - \frac{j0.5 V_1(t)}{-j20} = 40 \angle 0^\circ$$

$$\Rightarrow \frac{V_1(t)}{40} + \frac{jV_1(t)}{20} + \frac{V_1(t)}{40} = 40 \angle 0^\circ \Rightarrow \frac{V_1(t)}{20} + \frac{jV_1(t)}{20} = 40 \angle 0^\circ.$$

$$\Rightarrow V_1(t) \left( \frac{1+j}{20} \right) = 40 \angle 0^\circ \Rightarrow V_1(t) = \frac{800 \angle 0^\circ}{(1+j)}$$


$$\Rightarrow V_1(t) = 400(1-j) = 565.68 \angle -45^\circ \text{ Volt}$$

$$\text{From eq. iii), } V_2(t) = 0.5 \angle 90^\circ V_1(t) = 0.5 \times 565.68 \angle 90^\circ - 45^\circ$$

$$V_2(t) = 282.84 \angle 45^\circ \text{ Volt}$$

$$\Rightarrow V_1(t) = 565.68 \cos(\omega t - 45^\circ) \text{ V.}$$
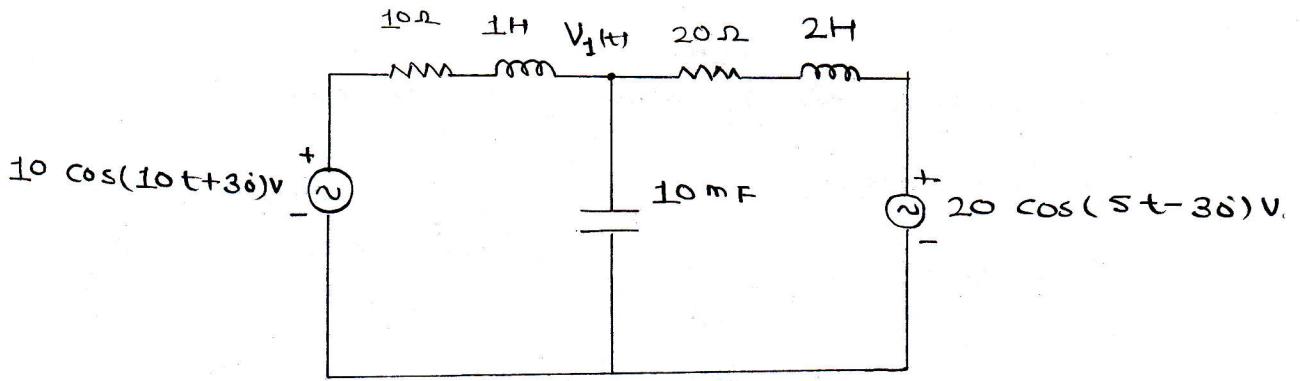
$$V_2(t) = 282.84 \cos(\omega t + 45^\circ) \text{ V.}$$



Applying Superposition Theorem:-


i) Take left <sup>voltage</sup> source only, right <sup>voltage</sup> source is shorted.

$$\therefore \omega = 10 \text{ rad/s}$$

The equivalent circuit  $\Rightarrow$

$$X_L = j\omega L = j10 \Omega$$
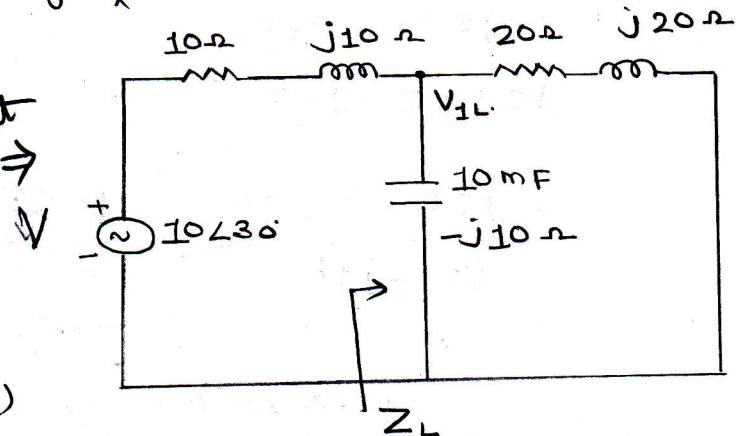
$$X_C = \frac{-j}{\omega C} = -j10 \Omega$$



$$\Rightarrow Z_L = (20 + j20) \parallel (-j10)$$

$$= \frac{(20 + j20) \times (-j10)}{(20 + j20 - j10)} = \frac{200 - j200}{(20 + j10)} = \frac{20(1-j)}{(2+j)}$$

$$\Rightarrow Z_L = \frac{20(1-j)(2-j)}{5} = 4[2-j-2j-1] = 4(1-3j) = 4-12j$$

By voltage division:

$$\Rightarrow V_{1L} = \frac{Z_L}{Z_L + 10 + j10} \times 10 \angle 30^\circ = \frac{(4-j12) \times 10 \angle 30^\circ}{4-j12+10+j10}$$

$$\Rightarrow V_{1L} = \frac{12.65 \angle -71.57^\circ \times 10 \angle 30^\circ}{14-j2} = \frac{126.5 \angle -41.57^\circ}{14.142 \angle -8.13^\circ}$$

$$V_{1L} = 8.944 \angle -33.44^\circ$$

$$V_{1L}(t) = 8.944 \cos(10t - 33.44) V$$


ii) Now take right <sup>Voltage</sup> source, shorted out left <sup>Voltage</sup> source.

$$\omega = 5 \text{ rad/s}$$

$$X_L = \omega L, X_C = \frac{1}{\omega C}$$

Equivalent Circuit
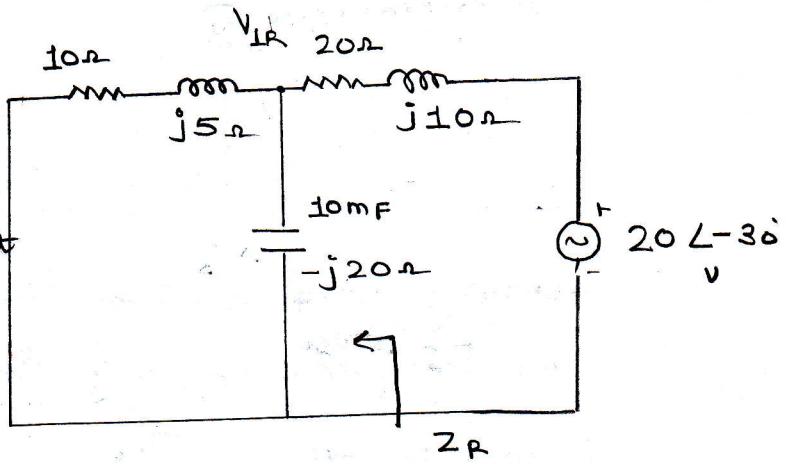
$$\Rightarrow Z_R = (10 + j5) \parallel (-j20) \Rightarrow$$



$$= \frac{(10 + j5) \times (-j20)}{10 + j5 - j20}$$

$$= \frac{-j200 + 100}{10 - j15} = \frac{(100 - j200)(10 + j15)}{100 + 225} = \frac{1}{325} [1000 - j2000 + j1500 + 3000] \\ = \frac{1}{325} [1000 - j500] = 12.3 - j1.536$$



$$\therefore V_{LR} = \frac{12.3 - j1.536}{12.3 - j1.536 + 20 + j10} \times 20 \angle -30^\circ = 12.4 \angle -7.12^\circ$$

$$= \frac{248 \angle -37.12^\circ}{33.38 \angle 14.67^\circ} = 7.43 \angle -51.8^\circ \text{ V}$$

$$V_{LR}(t) = 7.43 \cos(5t - 51.8^\circ) \text{ V}$$

$$\therefore \text{Net } V_L(t) = V_{LL}(t) + V_{LR}(t)$$
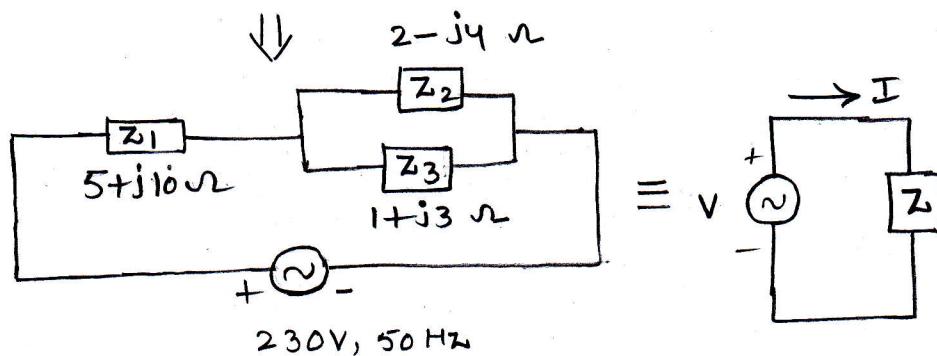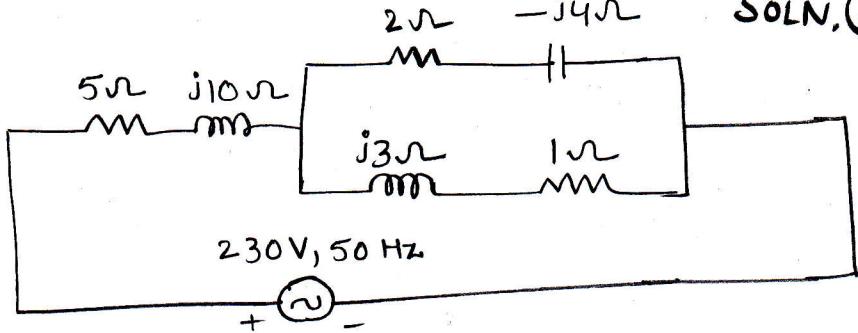
$$= 8.94 + \cos(10t - 33.44) + 7.43 \cos(5t - 51.8^\circ) \text{ V}$$



Here,

$$Z = Z_1 + (Z_2 \parallel Z_3) = Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3}$$

$$= 5 + j10 + \frac{(2-j4)(1+j3)}{2-j4 + 1+j3}$$

$$= 5 + 10j + \frac{14 + 2j}{3-j} = 5 + 10j + \frac{(14+2j)(3+j)}{10}$$

$$= 5 + 10j + 4 + 2j = 9 + j12 \Omega$$

&  $V_{rms} = 230 V$

Then,

$$I_{rms} = \frac{V_{rms}}{Z} = \frac{230}{9+j12} = \frac{230(9-j12)}{225} = 9.2 - j12.27$$

$$= 15.33 \angle -53.13^\circ \text{ Amp}$$

which implies that  $\Rightarrow \theta = 53.13^\circ$

$$\therefore \text{Average Power, } P_{avg} = V I_{rms} \cos \theta = 230 \times 15.33 \times \cos 53.13^\circ$$


$$= 2115.54 \text{ W}$$

$$\text{Reactive Power, } P_{react} = V I_{rms} \sin \theta = 230 \times 15.33 \times \sin 53.13^\circ$$

$$= 2820.72 \text{ W}$$

$$\omega = 4 \text{ k rad/s.}$$

$$Z_{in} = jX \parallel (5-j8)$$

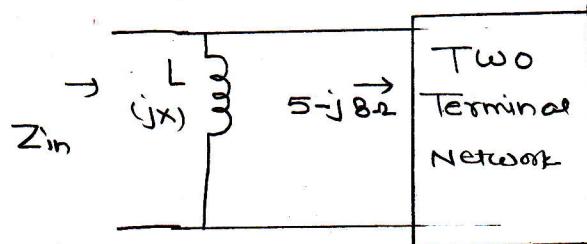

a)  $Z_{in} = \frac{(jX) \times (5-j8)}{5-j8+jX}$

$$= \frac{8X + j5X}{5 + j(X-8)} = \frac{8X + j5X}{5 + j(X-8)} \times \frac{5 - j(X-8)}{5 - j(X-8)}$$

$$= \frac{1}{25 + (X-8)^2} [40X + j25X - j8X(X-8) + 5X(X-8)] = R_{in} + jX_{in}$$

Now,  $X_{in} = 0$  for zero reactance in input impedance.

$$\Rightarrow 25X - 8X(X-8) = 0 \Rightarrow 25 = 8(X-8) [\because X \neq 0]$$

$$\Rightarrow X = 8 + \frac{25}{8} = 11.125 \Omega$$

$$L = \frac{X}{\omega} = \frac{11.125}{4000} \text{ H} = 2.781 \text{ mH}$$

b)  $|Z_{in}| = 4 \quad \left[ \because Z_{in} = \frac{8X + j5X}{5 + j(X-8)} \right]$


$$\Rightarrow \frac{64X^2 + 25X^2}{25 + (X-8)^2} = 4^2$$

$$\Rightarrow \frac{89X^2}{X^2 - 16X + 89} = 16 \Rightarrow 73X^2 + 256X - 1424 = 0$$

$$\Rightarrow X = 2.9986, -6.505$$


$\Rightarrow X = 2.9986 \Omega$  ( $\because$  Inductance has to be placed parallel to the network, so only positive X is taken)
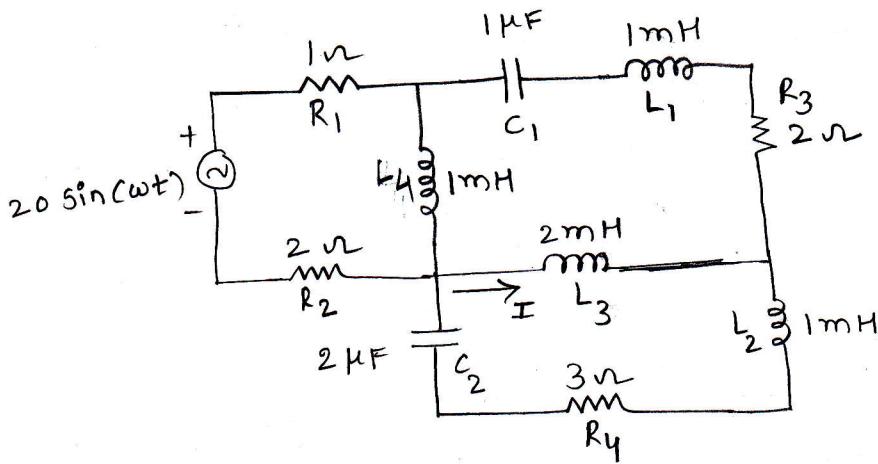
$$\Rightarrow L = \frac{X}{\omega} = 0.7496 \text{ mH}$$



$$\omega = 10,000 \text{ rad/s}$$

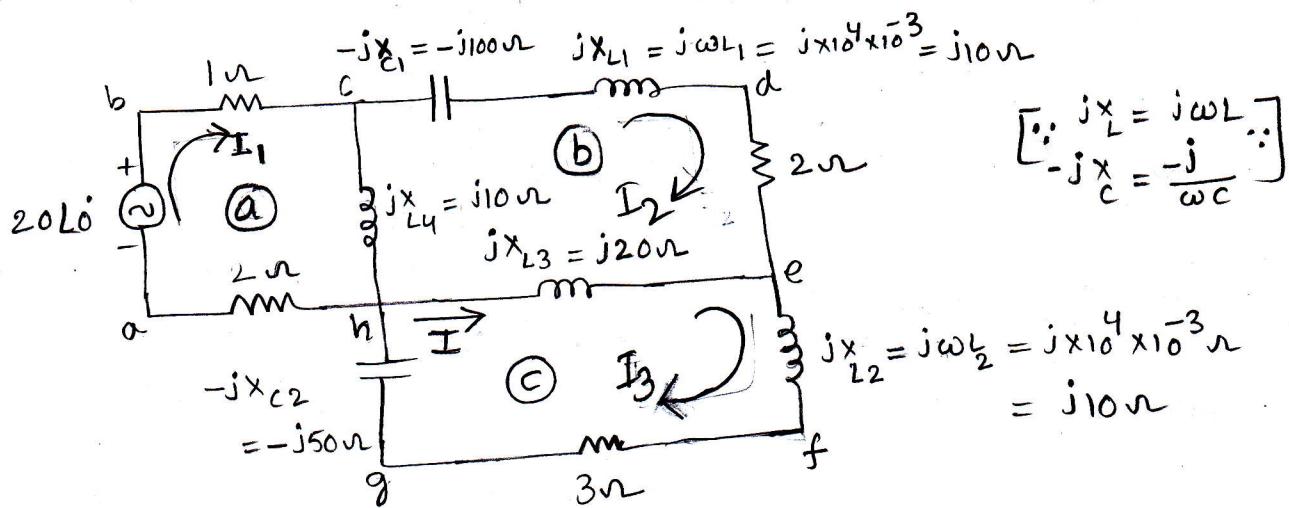By converting capacitors and inductors into their equivalent impedances, we get the following circuit



NOW writing the loop equations,  
Applying KVL in loop abcda gives,

$$-20 + I_1 + j10(I_1 - I_2) + 2I_1 = 0$$

$$\Rightarrow (3+10j)I_1 - j10I_2 = 20 \quad \textcircled{1}$$

Applying KVL in loop cdehc gives,

$$(-j100 + j10 + 2)I_2 + j20(I_2 - I_3) + j10(I_2 - I_1) = 0$$

$$\Rightarrow -j10I_1 + (2-j60)I_2 - j20I_3 = 0 \quad \textcircled{2}$$

Applying KVL in loop efghe gives,

$$(j10 + 3 - j50)I_3 + j20(I_3 - I_2) = 0$$

$$\Rightarrow -j20I_2 + (3-j20)I_3 = 0 \quad \textcircled{3}$$

$$\Rightarrow I_2 = \left( \frac{3-j20}{j20} \right) I_3 = (-1-j0.15)I_3 \quad \textcircled{4}$$

from eqn ① we can write that,

P-8

$$I_1 = \frac{20 + j10 I_2}{3 + 10j} \quad \text{--- } ⑤$$

Putting ⑤ in ③,

$$-j10 \left( \frac{20 + j10 I_2}{3 + 10j} \right) + (2 - j60) I_2 - j20 \frac{I_2}{3} = 0$$

$$\Rightarrow I_2 \left[ 2 - j60 + \frac{100}{3 + 10j} \right] - j20 \frac{I_2}{3} = \frac{200j}{3 + 10j}$$

$$\Rightarrow I_2 (2 - j60 + 2.752 - j9.174) - j20 \frac{I_2}{3} = 18.35 + j5.5$$

$$\Rightarrow I_2 (4.752 - j69.174) - 20j I_3 = 18.35 + j5.5 \quad \text{--- } ⑥$$

Putting ④ into ⑥,

$$\Rightarrow -20j I_3 + (4.752 - j69.174) (-1 - j0.15) I_3 = 18.35 + j5.5$$

$$\Rightarrow -20j I_3 + (-15.128 + j68.46) I_3 = 18.35 + j5.5$$

$$\Rightarrow I_3 = \frac{18.35 + j5.5}{-15.128 + j68.46} = -4.293 \times 10^{-3} - j0.377 \text{ A.}$$

Then from ④,

$$I_2 = (-1 - j0.15) \times (-4.293 \times 10^{-3} - j0.377)$$


$$= -0.0523 + j0.378 \text{ A.}$$

Now the desired current is,

$$I = I_3 - I_2 = -4.293 \times 10^{-3} - j0.377 + 0.0523 - j0.378$$

$$= 0.048 - j0.755 = 0.756 \angle -86.36^\circ \text{ A.}$$
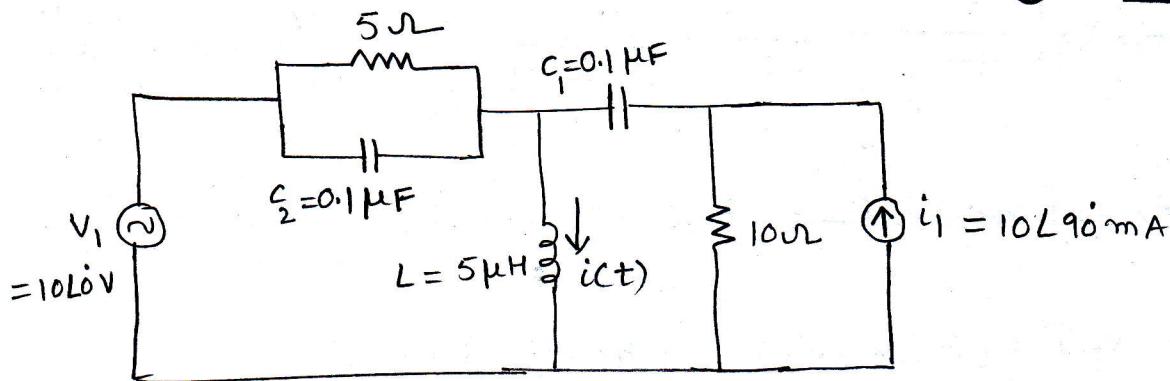
$$\therefore I = 0.756 \angle -86.36^\circ \text{ A}$$




$$\omega = 10^6 \text{ rad/s}$$


$$X_L = \omega L = 10^6 \times 5 \times 10^{-6} = 5 \Omega$$

$$X_C = \frac{1}{\omega C_i} = \frac{1}{10^6 \times 0.1 \times 10^{-6}} = 10\Omega \quad (\because i=1,2)$$

Then the circuit reduces to,

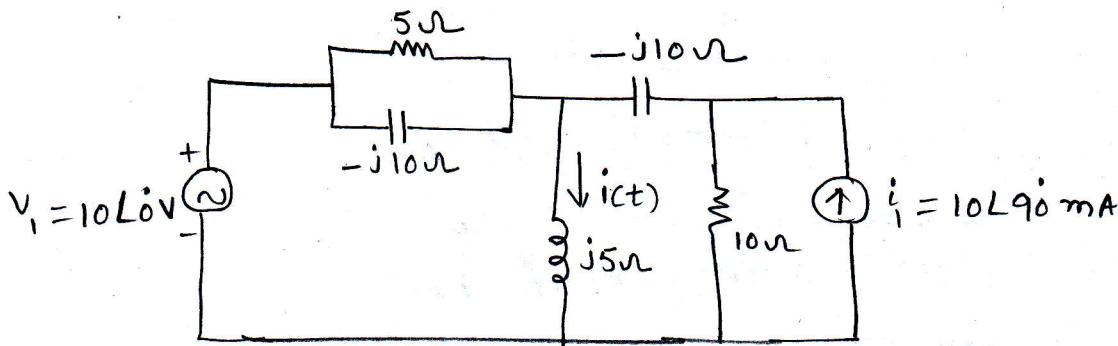

↓ (from Source Transformation Theorem)

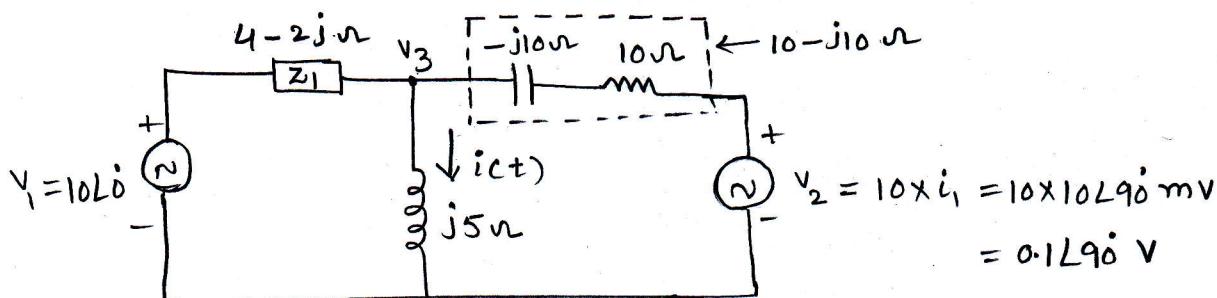

$$\text{Here } Z_1 = 5 \parallel (-j10) = \frac{5 \times -10j}{5 - 10j} = 4 - 2j \Omega$$

Using the nodal analysis for the above circuit, we write that

$$\frac{v_3 - 10L90^\circ}{4 - 2j} + \frac{v_3}{5j} + \frac{v_3 - 0.1L90^\circ}{10 - 10j} = 0$$

$$\Rightarrow V_3 \left[ \frac{1}{4-2j} + \frac{1}{5j} + \frac{1}{10-j10} \right] = \frac{10\angle 0^\circ}{4-j2} + \frac{0.1\angle 90^\circ}{10-j10}$$

$$\Rightarrow V_3 [0.2 + 0.1j - 0.2j + 0.05 + 0.05j] = 2 + j1 - 5 \times 10^{-3} + j5 \times 10^{-3}$$


$$\Rightarrow V_3 (0.25 - 0.05j) = 1.995 + j1.005$$

$$\Rightarrow V_3 = \frac{1.995 + j1.005}{0.25 - 0.05j} = 6.9 + j5.4 \text{ Volts}$$

Now,

$$\begin{aligned} i(t) &= \frac{V_3}{j5} = \frac{6.9 + j5.4}{j5} \\ &= 1.08 - j1.38 \\ &= 1.753 \angle -51.95^\circ \text{ Amp.} \end{aligned}$$
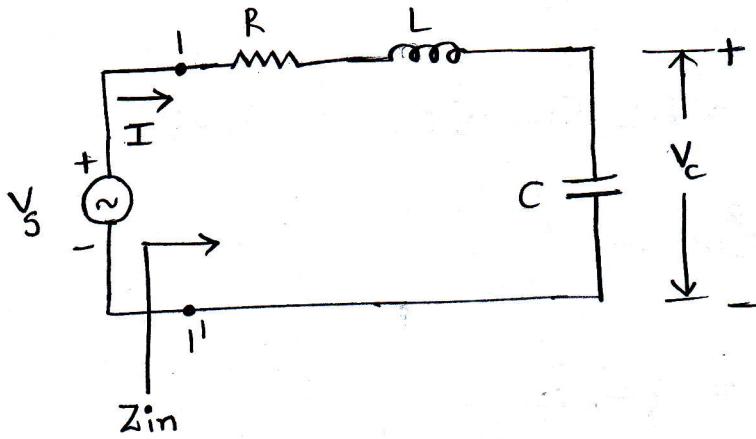
$$\boxed{i(t) = 1.753 \angle -51.95^\circ \text{ Amp}}$$



impedance looking at the terminals 1-1 is,

$$Z_{in} = R + j\left[\omega L - \frac{1}{\omega C}\right]$$

$$\Rightarrow |Z_{in}| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

from the figure,

$$|I| = \frac{|V_s|}{|Z_{in}|} = \frac{|V_s|}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

(a) voltage across the capacitor is,

$$|V_c| = |j\chi_c| \cdot |I| = \frac{|V_s|}{\omega C \left[ \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \right]}$$

$$= \frac{|V_s|}{\sqrt{R^2 \omega^2 C^2 + (\omega^2 LC - 1)^2}}$$

$|V_c|$  is maximum when,

$$\frac{d|V_c|}{d\omega} \Big|_{\omega=\omega_c} = 0$$

$$\Rightarrow \frac{d|V_c|}{d\omega} \Big|_{\omega=\omega_c} = -\frac{1}{2} \cdot \frac{|V_s| \left[ 2\omega_c^2 R^2 C^2 + 2(\omega_c^2 LC - 1) \cdot 2\omega_c^2 LC \right]}{\left[ R^2 \omega_c^2 C^2 + (\omega_c^2 LC - 1)^2 \right]^{3/2}} = 0$$

$$\Rightarrow 2\omega_c^2 R^2 C^2 + 2(\omega_c^2 LC - 1) \cdot 2\omega_c^2 LC = 0$$

$$\Rightarrow 2\omega_c^2 R^2 C^2 = 4\omega_c^2 LC (1 - \omega_c^2 LC)$$

$$\Rightarrow R^2 C = 2L \left(1 - \omega_c^2 LC\right) [\because \omega_c \neq 0]$$

$$\Rightarrow 1 - \omega_c^2 LC = \frac{R^2 C}{2L}$$

$$\Rightarrow \omega_c^2 LC = 1 - \frac{R^2 C}{2L}$$

$$\Rightarrow \omega_c^2 = \frac{1}{LC} - \frac{R^2}{2L^2}$$

$$\Rightarrow \omega_c = 2\pi f_c = \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$$\therefore f_c = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}} \text{ Hz.}$$

(b) Voltage across the inductor,

$$|V_L| = |jx_L| \cdot |I| = \frac{\omega L \cdot |V_s|}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$|V_L| \text{ is maximum when } \frac{d|V_L|}{d\omega} \Big|_{\omega=\omega_L} = 0$$

$$\Rightarrow \frac{d|V_L|}{d\omega} \Big|_{\omega=\omega_L} = \frac{L \cdot |V_s|}{\sqrt{R^2 + (\omega_L - \frac{1}{\omega_C})^2}} - \frac{\omega_L |V_s| \cdot 2 \left[ \omega_L - \frac{1}{\omega_C} \right] \left[ L + \frac{1}{\omega_L^2 C} \right]}{2 \left[ R^2 + (\omega_L - \frac{1}{\omega_C})^2 \right]^{3/2}}$$

$$\Rightarrow \frac{L |V_s|}{\sqrt{R^2 + (\omega_L - \frac{1}{\omega_C})^2}} = \frac{\omega_L |V_s| \left[ \omega_L - \frac{1}{\omega_L} \right] \left[ L + \frac{1}{\omega_L^2 C} \right]}{\left[ R^2 + (\omega_L - \frac{1}{\omega_C})^2 \right]^{3/2}}$$

$$\Rightarrow R^2 + \left(\omega_L - \frac{1}{\omega_C}\right)^2 = \left(\omega_L - \frac{1}{\omega_C}\right)\left(\omega_L + \frac{1}{\omega_C}\right)$$

$$\Rightarrow R^2 + \omega_L^2 L^2 + \frac{1}{\omega_L^2 C^2} - \frac{2L}{C} = \omega_L^2 L^2 - \frac{1}{\omega_L^2 C^2}$$

$$\Rightarrow -R^2 + \frac{2L}{C} = \frac{2}{\omega_L^2 C^2}$$

$$\Rightarrow \omega_L^2 C^2 = \frac{2}{\frac{2L}{C} - R^2}$$

$$\Rightarrow \omega_L^2 = \frac{1}{LC - \frac{R^2 C^2}{2}}$$

$$\Rightarrow \omega_L = 2\pi f_L = \frac{1}{\sqrt{LC - \frac{R^2 C^2}{2}}}$$

$$\therefore f_L = \frac{1}{2\pi \sqrt{LC - \frac{R^2 C^2}{2}}} \text{ Hz}$$